

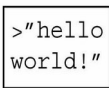

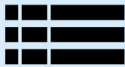
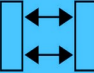
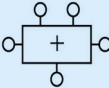
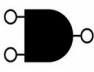
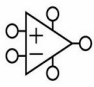


Chapter 7

Digital Design and Computer Architecture, 2nd Edition

David Money Harris and Sarah L. Harris

Chapter 7 :: Topics

- Introduction
- State elements of MIPS Processor
- Design Process & Performance Analysis of Single Cycle Processor
- Single-Cycle Data path
- Single cycle control for R-type A/L instrns
- Design Process & Performance Analysis of Multi cycle Processor
- Multicycle Data path
- Multi cycle control for R-type A/L instrns

| | |
|----------------------|---|
| Application Software |  |
| Operating Systems |  |
| Architecture |  |
| Micro-architecture |  |
| Logic |  |
| Digital Circuits |  |
| Analog Circuits |  |
| Devices |  |
| Physics |  |

Introduction

- **Microarchitecture:** how to implement an architecture in hardware.
- Processor:
 - **Datapath(32 bit):** functional blocks
 - ✓ memories, registers, ALUs, mux
 - **Control:** control signals
 - Receives current instruction from datapath & tells datapath how to execute that instruction.
 - ✓ Mux select, register enable, memory write signals
- Computer Architecture:
 - Instruction set
 - Architectural state
 - ✓ PC and 32 registers

| | |
|----------------------|---------------------------|
| Application Software | programs |
| Operating Systems | device drivers |
| Architecture | instructions registers |
| Micro-architecture | datapaths controllers |
| Logic | adders memories |
| Digital Circuits | AND gates NOT gates |
| Analog Circuits | amplifiers filters |
| Devices | transistors diodes |
| Physics | electrons |



Microarchitecture

- Multiple implementations for a single architecture:
 - **Single-cycle:** Each instruction executes in a single cycle. no nonarchitectural state. cycle time is limited by the slowest instruction.
 - **Multicycle:** Each instruction is broken into series of shorter cycles. reduces hardware cost by reusing expensive hardware blocks adders/memories. cycle time limited by slowest functional unit.

Processor Performance

- Performance measured by program execution time

Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)

- Definitions:
 - CPI: Cycles/instruction
 - clock period: seconds/cycle
 - IPC: instructions/cycle = IPC
- Challenge is to satisfy constraints of:
 - Cost
 - Power
 - Performance


MIPS Processor

- Consider subset of MIPS instructions:
 - R-type instructions: `and`, `or`, `add`, `sub`, `slt`
 - Memory instructions: `lw`, `sw`
 - Branch instructions: `beq`

Architectural State

- Determines everything about a processor:
 - PC
 - 32 registers
 - Memory

MIPS State Elements

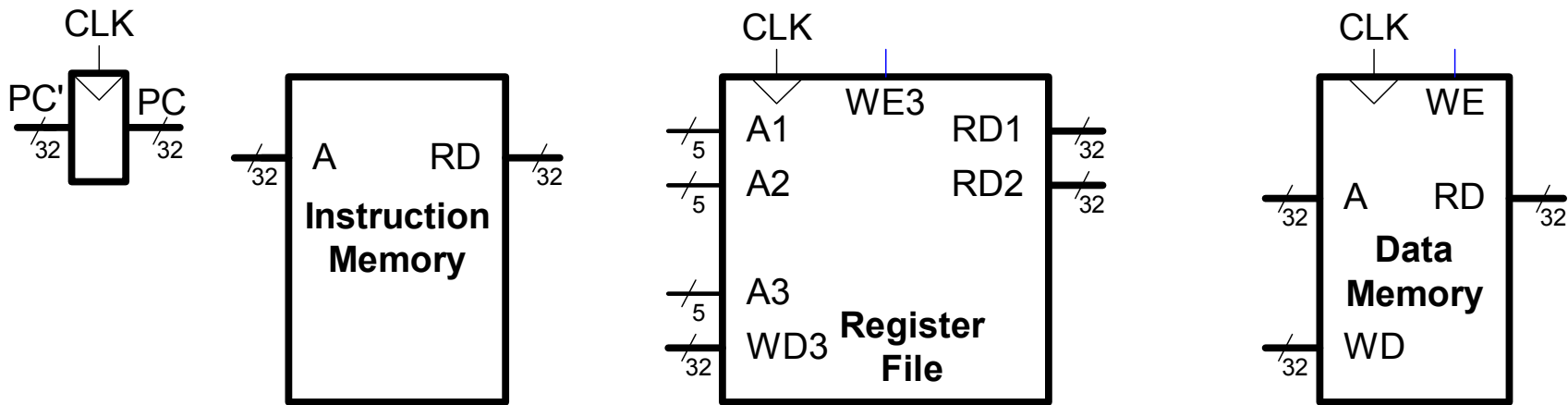


Single-Cycle MIPS Processor

- Datapath
- Control

Single-Cycle Datapath: l_w fetch

STEP 1: Fetch instruction

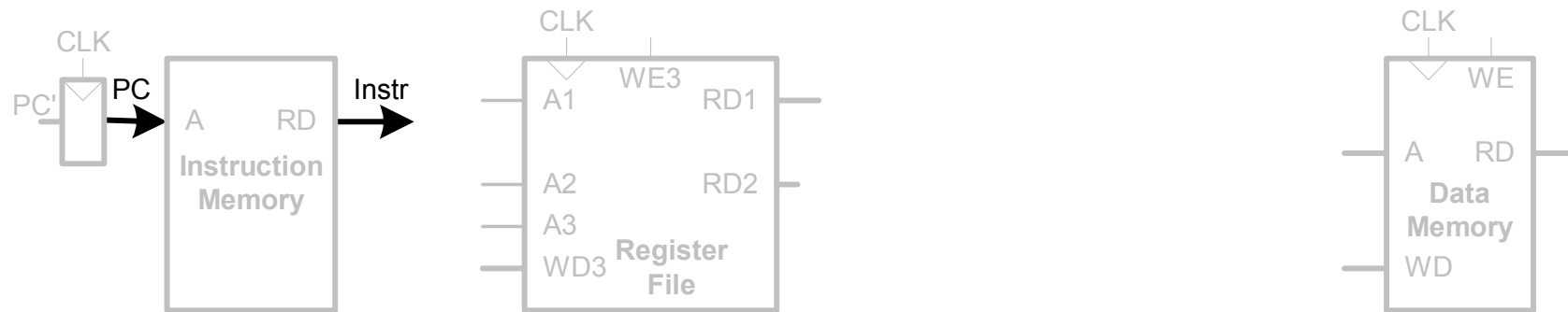


A1-rs

A2-rt(sw)

A3-rt(lw)


Single-Cycle Datapath: 1_W Immediate

STEP 3: Sign-extend the immediate

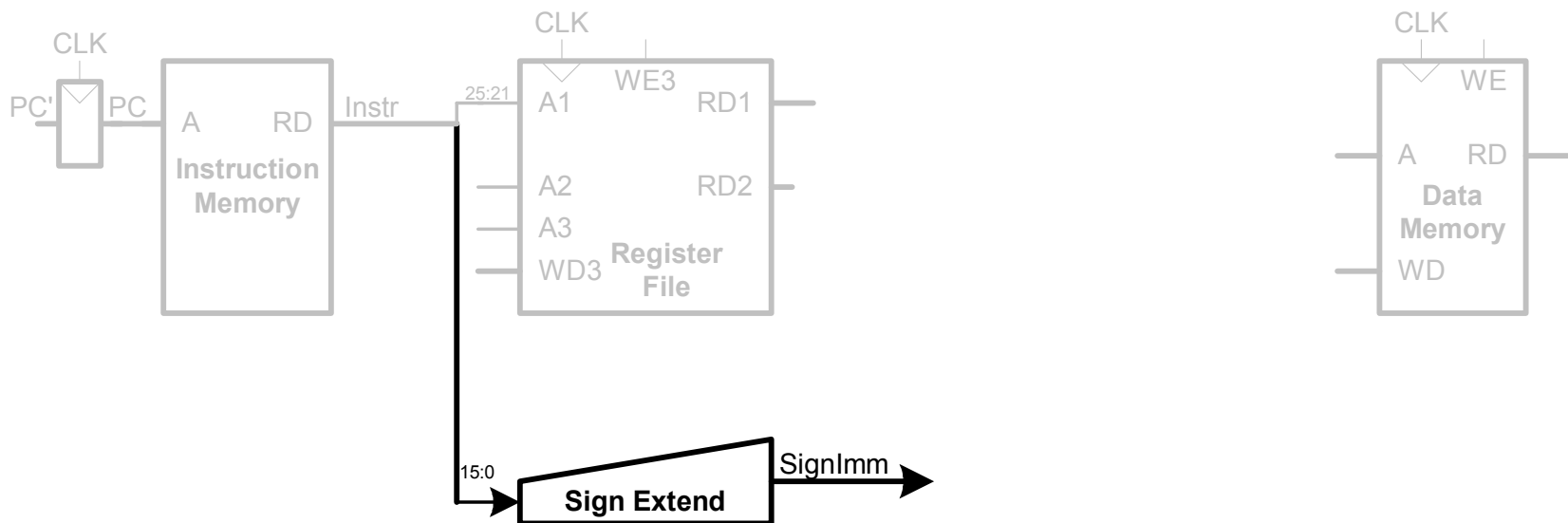


Single-Cycle Datapath: 1_w address

STEP 4: Compute the memory address

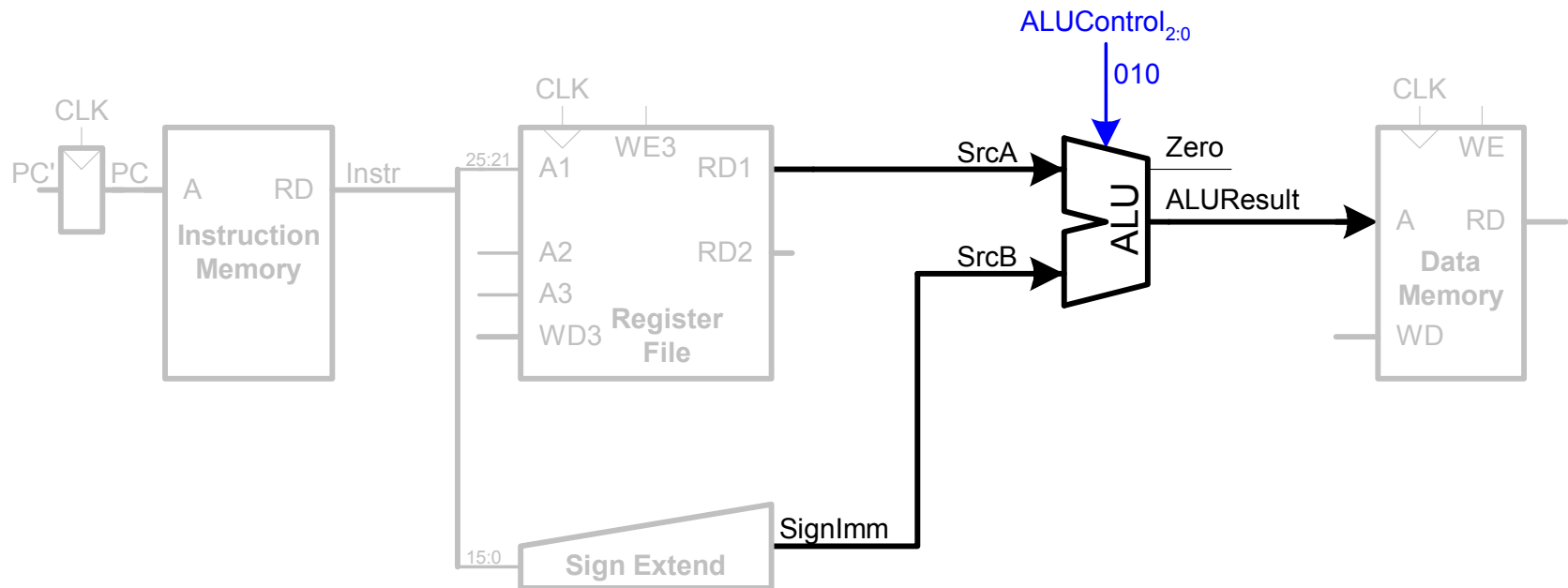


Single-Cycle Datapath: 1_W Memory Read

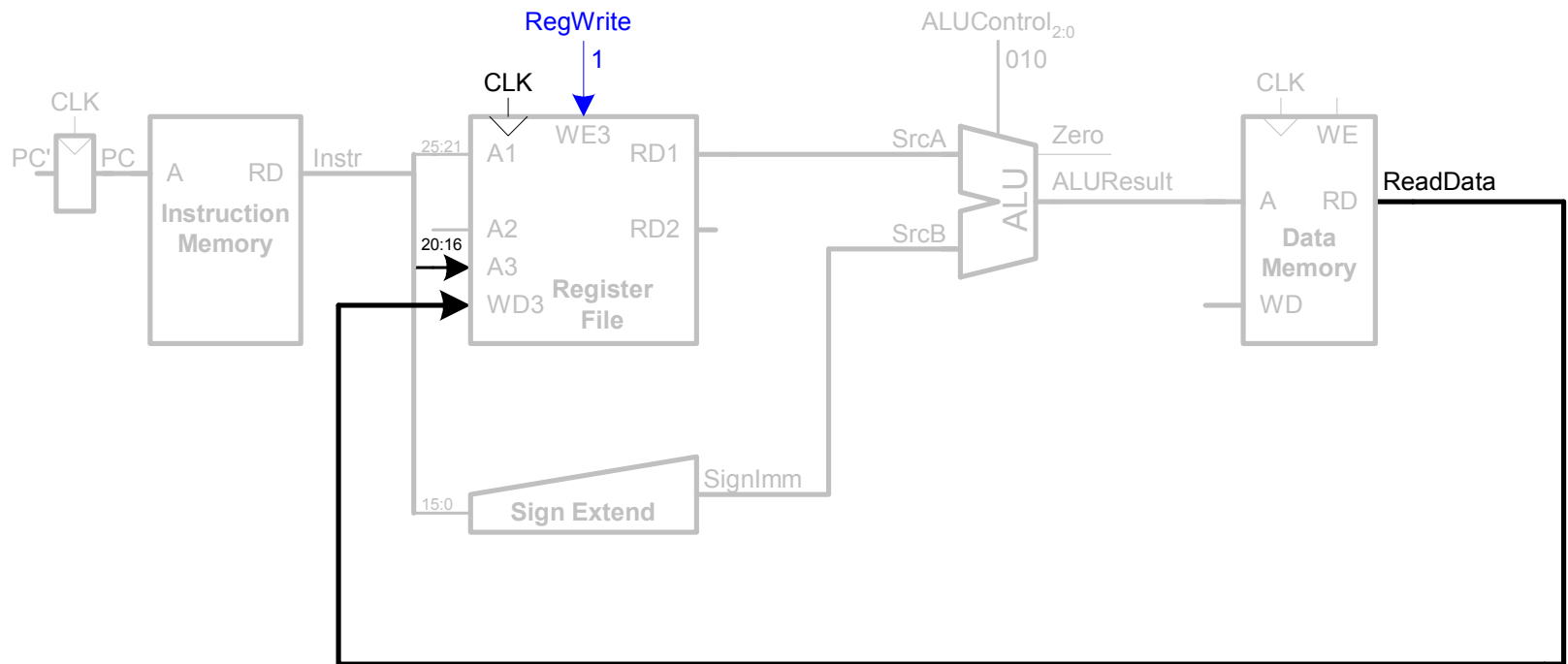- **STEP 5:** Read data from memory and write it back to register file




Single-Cycle Datapath: 1_W PC Increment

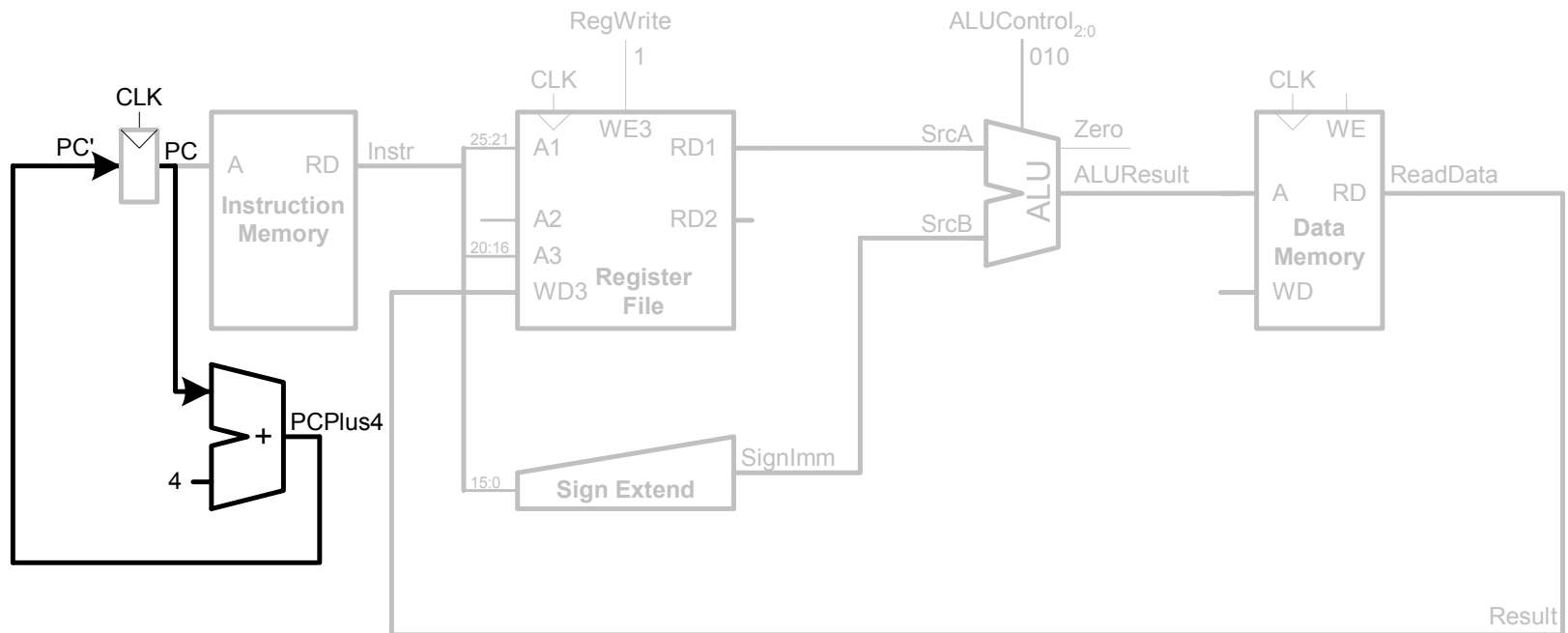STEP 6: Determine address of next instruction




Single-Cycle Datapath: sw

Write data in rt to memory

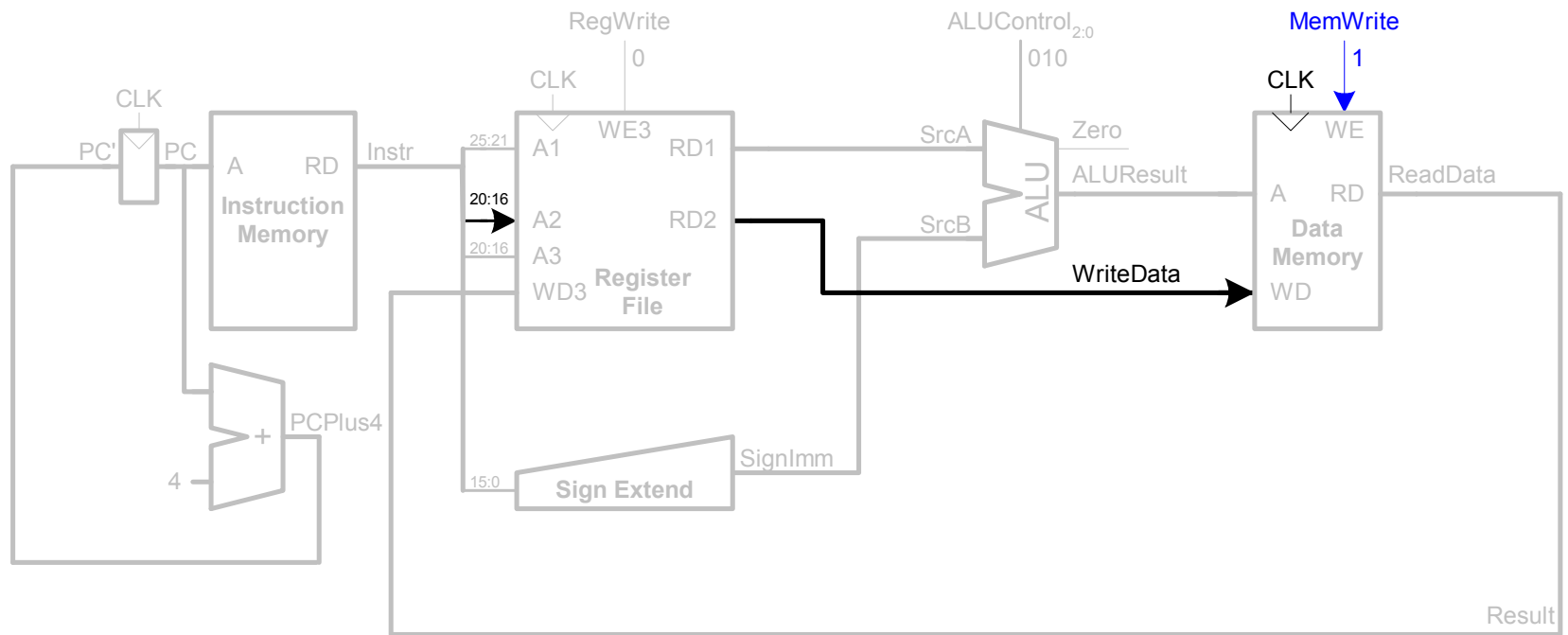

Single-Cycle Datapath: R-Type

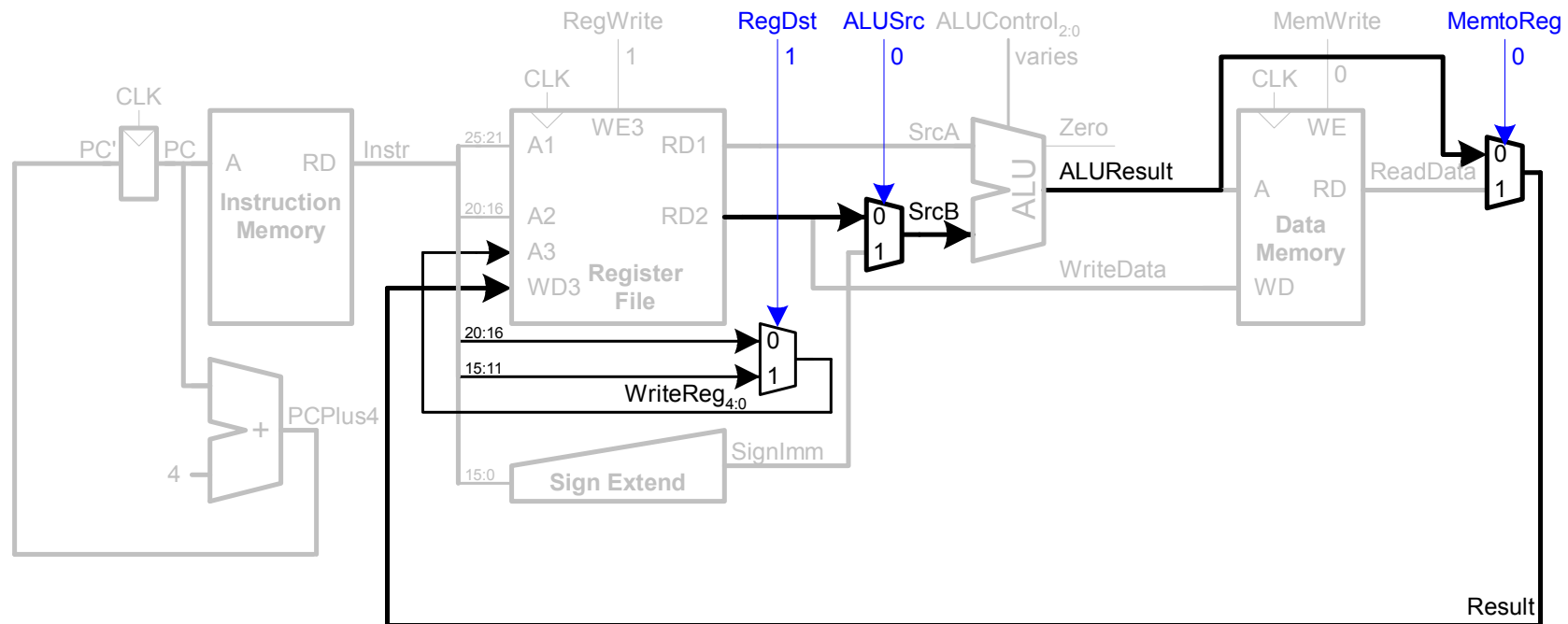
- Read from `rs` and `rt`
- Write `ALUResult` to register file
- Write to `rd` (instead of `rt`)




Single-Cycle Datapath: beq

- Determine whether values in rs and rt are equal
- Calculate branch target address:

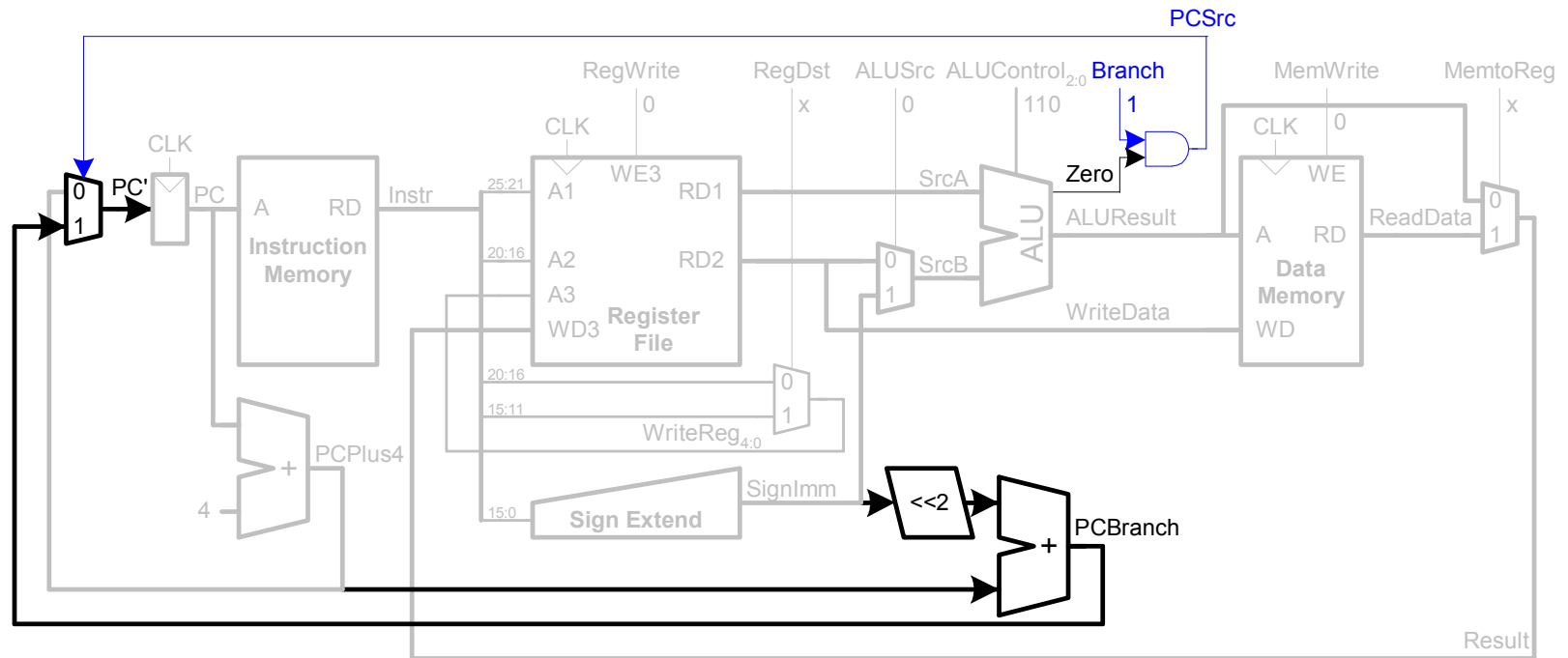
$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC}+4)$$




Single-Cycle Processor

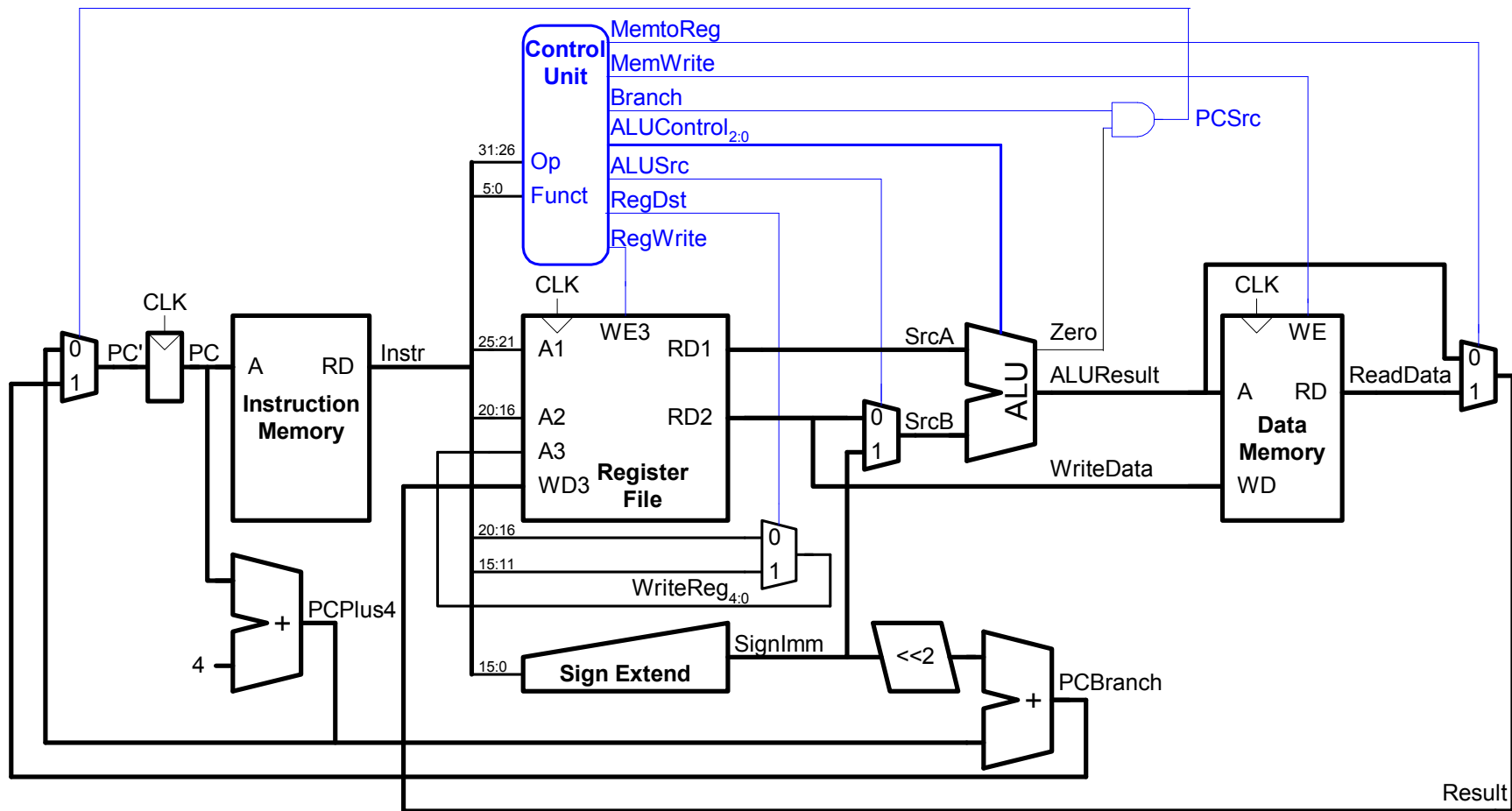

Single-Cycle Control

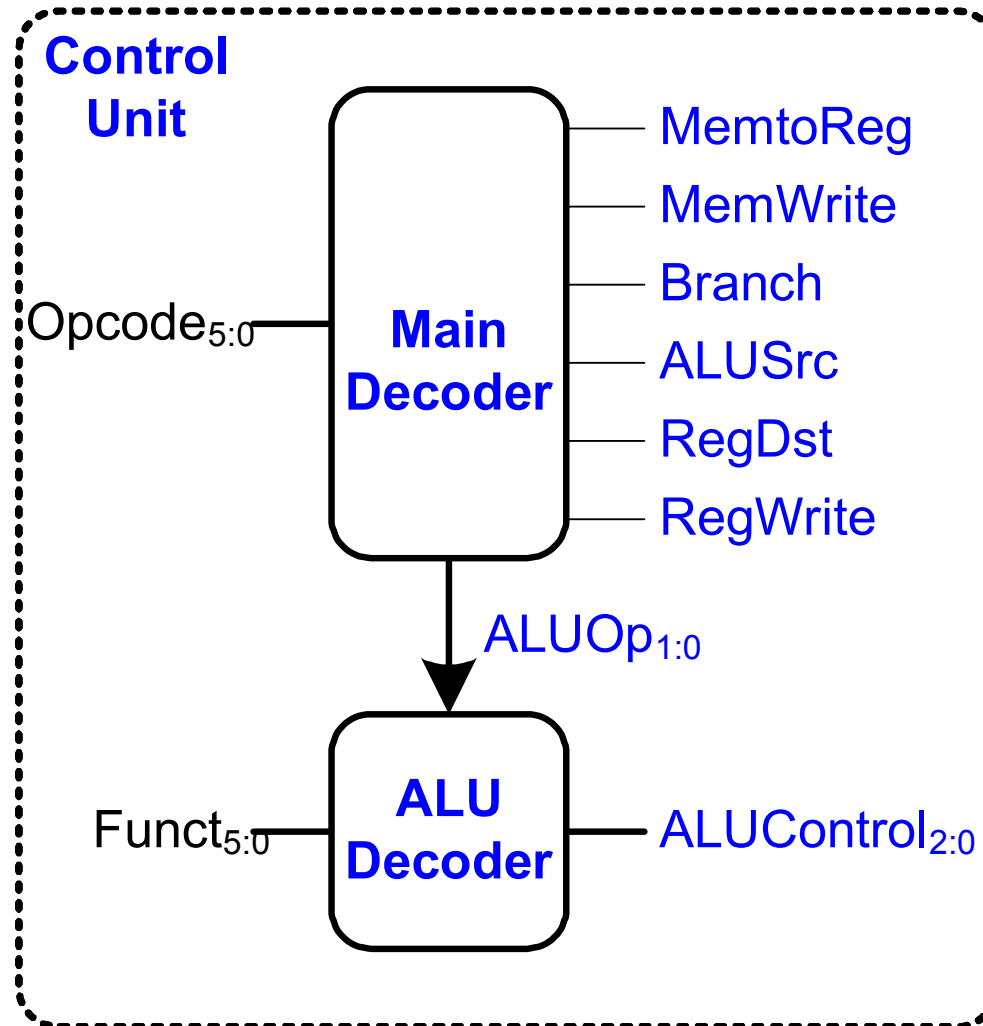


Review: ALU

 

| $F_{2:0}$ | Function |
|-----------|---------------|
| 000 | $A \& B$ |
| 001 | $A B$ |
| 010 | $A + B$ |
| 011 | not used |
| 100 | $A \& \sim B$ |
| 101 | $A \sim B$ |
| 110 | $A - B$ |
| 111 | SLT |

Review: ALU

 


Control Unit: ALU Decoder

| ALUOp _{1:0} | Meaning |
|----------------------|---------------|
| 00 | Add |
| 01 | Subtract |
| 10 | Look at Funct |
| 11 | Not Used |

| ALUOp _{1:0} | Funct | ALUControl _{2:0} |
|----------------------|--------------|---------------------------|
| 00 | X | 010 (Add) |
| X1 | X | 110 (Subtract) |
| 1X | 100000 (add) | 010 (Add) |
| 1X | 100010 (sub) | 110 (Subtract) |
| 1X | 100100 (and) | 000 (And) |
| 1X | 100101 (or) | 001 (Or) |
| 1X | 101010 (slt) | 111 (SLT) |

Control Unit Main Decoder


| Instruction | Op _{5:0} | RegWrite | RegDst | AluSrc | Branch | MemWrite | MemtoReg | ALUOp _{1:0} |
|-------------|-------------------|----------|--------|--------|--------|----------|----------|----------------------|
| R-type | 000000 | | | | | | | |
| lw | 100011 | | | | | | | |
| sw | 101011 | | | | | | | |
| beq | 000100 | | | | | | | |

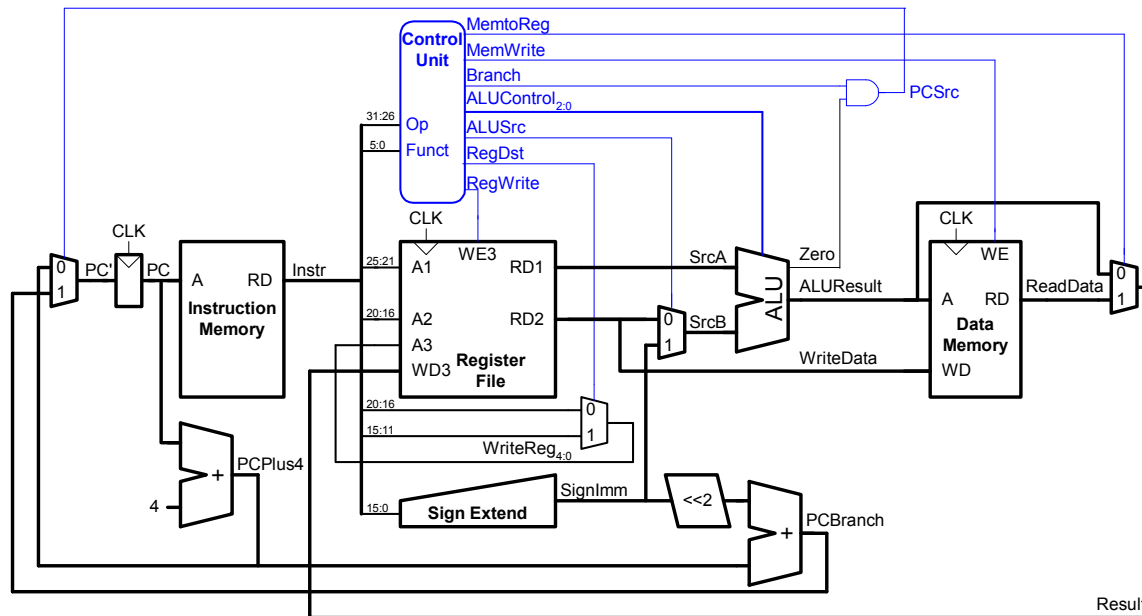


Control Unit: Main Decoder

| Instruction | Op _{5:0} | RegWrite | RegDst | AluSrc | Branch | MemWrite | MemtoReg | ALUOp _{1:0} |
|-------------|-------------------|----------|--------|--------|--------|----------|----------|----------------------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 0 | 00 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 |

Single-Cycle Datapath: Op r

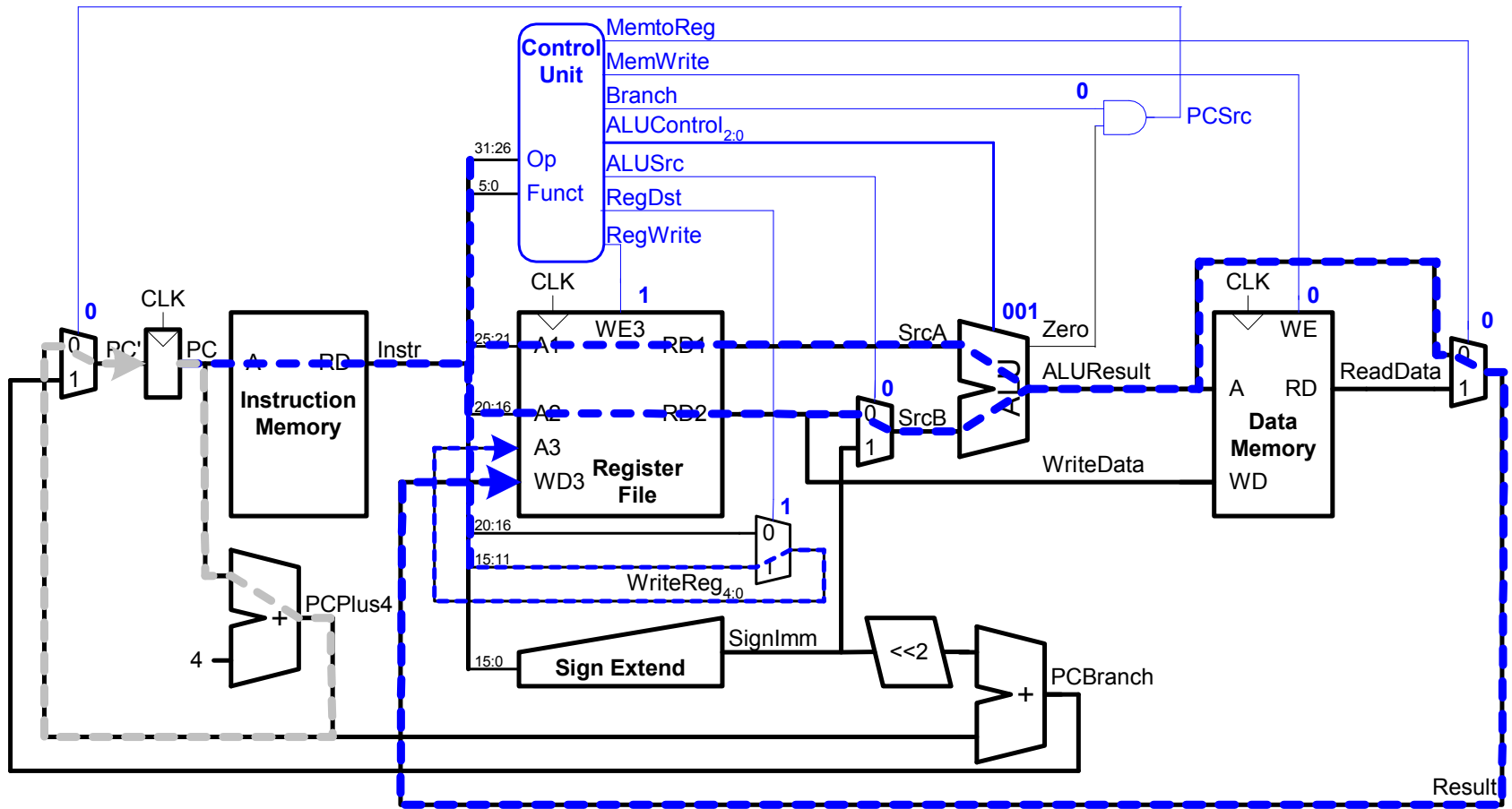

Extended Functionality: addi

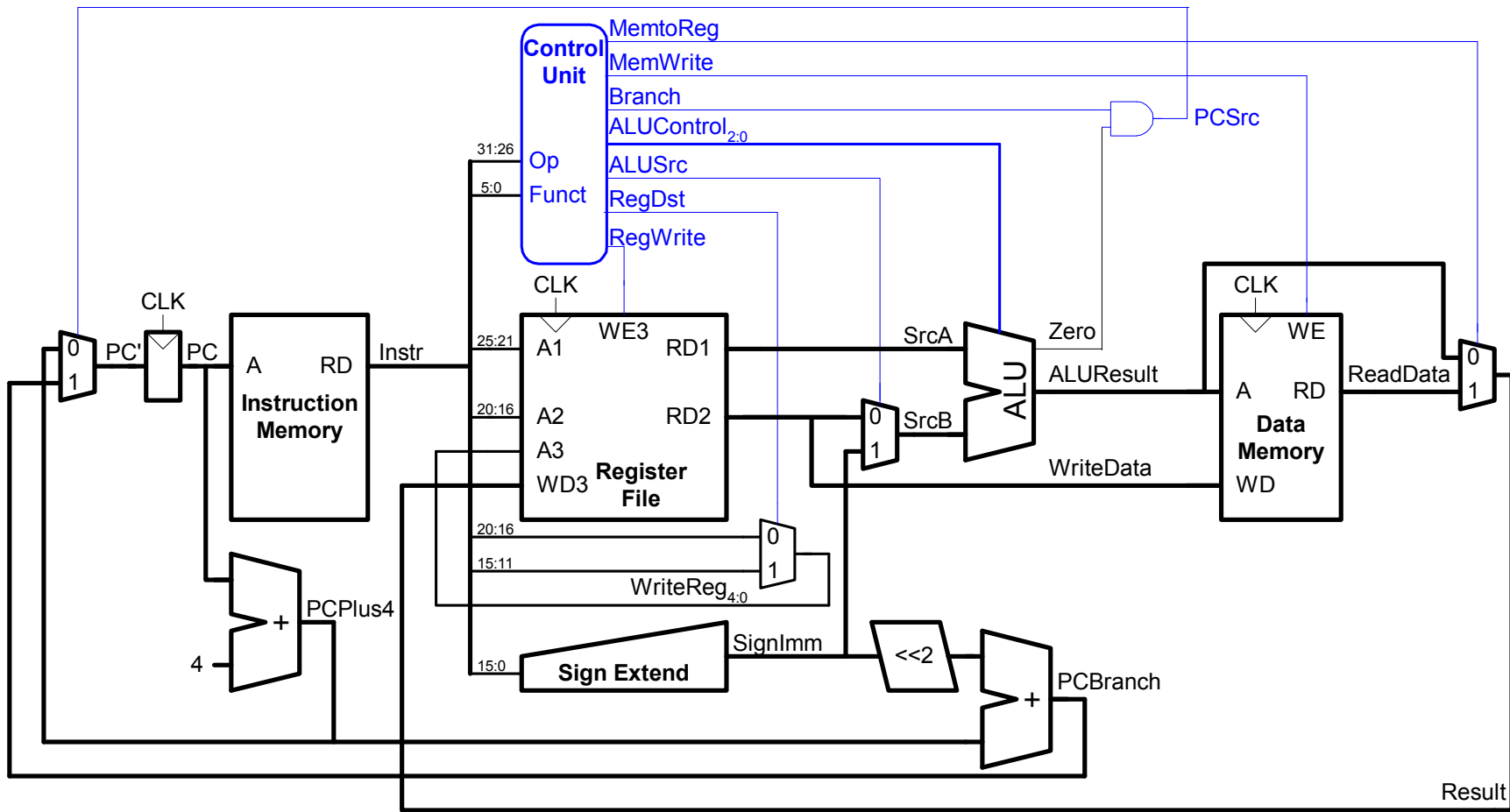

No change to datapath


Control Unit: addi

| Instruction | Op _{5:0} | RegWrite | RegDst | AluSrc | Branch | MemWrite | MemtoReg | ALUOp _{1:0} |
|-------------|-------------------|----------|--------|--------|--------|----------|----------|----------------------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 |
| addi | 001000 | | | | | | | |

Control Unit: addi

| Instruction | Op _{5:0} | RegWrite | RegDst | AluSrc | Branch | MemWrite | MemtoReg | ALUOp _{1:0} |
|-------------|-------------------|----------|----------|----------|----------|----------|----------|----------------------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 |
| addi | 001000 | 1 | 0 | 1 | 0 | 0 | 0 | 00 |

Extended Functionality: j

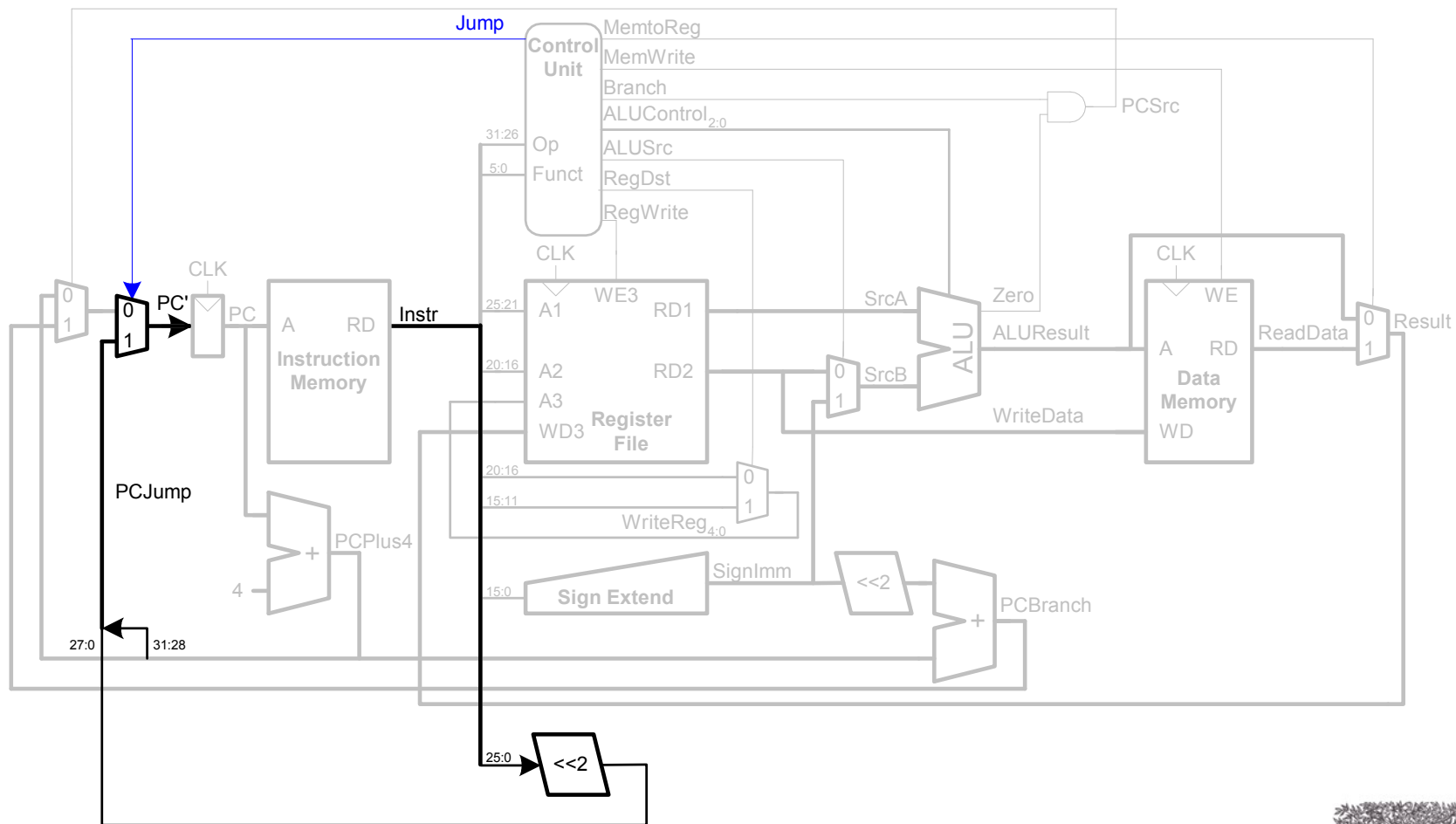

Control Unit: Main Decoder

| Instruction | Op _{5:0} | RegWrite | RegDst | AluSrc | Branch | MemWrite | MemtoReg | ALUOp _{1:0} | Jump |
|-------------|-------------------|----------|--------|--------|--------|----------|----------|----------------------|------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 | 0 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 | 0 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 | 0 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 | 0 |
| j | 000100 | | | | | | | | |

Control Unit: Main Decoder

| Instruction | Op _{5:0} | RegWrite | RegDst | AluSrc | Branch | MemWrite | MemtoReg | ALUOp _{1:0} | Jump |
|-------------|-------------------|----------|--------|--------|--------|----------|----------|----------------------|------|
| R-type | 000000 | 1 | 1 | 0 | 0 | 0 | 0 | 10 | 0 |
| lw | 100011 | 1 | 0 | 1 | 0 | 0 | 1 | 00 | 0 |
| sw | 101011 | 0 | X | 1 | 0 | 1 | X | 00 | 0 |
| beq | 000100 | 0 | X | 0 | 1 | 0 | X | 01 | 0 |
| j | 000100 | 0 | X | X | X | 0 | X | XX | 1 |


Review: Processor Performance

Program Execution Time

$$= (\# \text{instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

$$= \# \text{ instructions} \times \text{CPI} \times T_c$$

Single-Cycle Performance

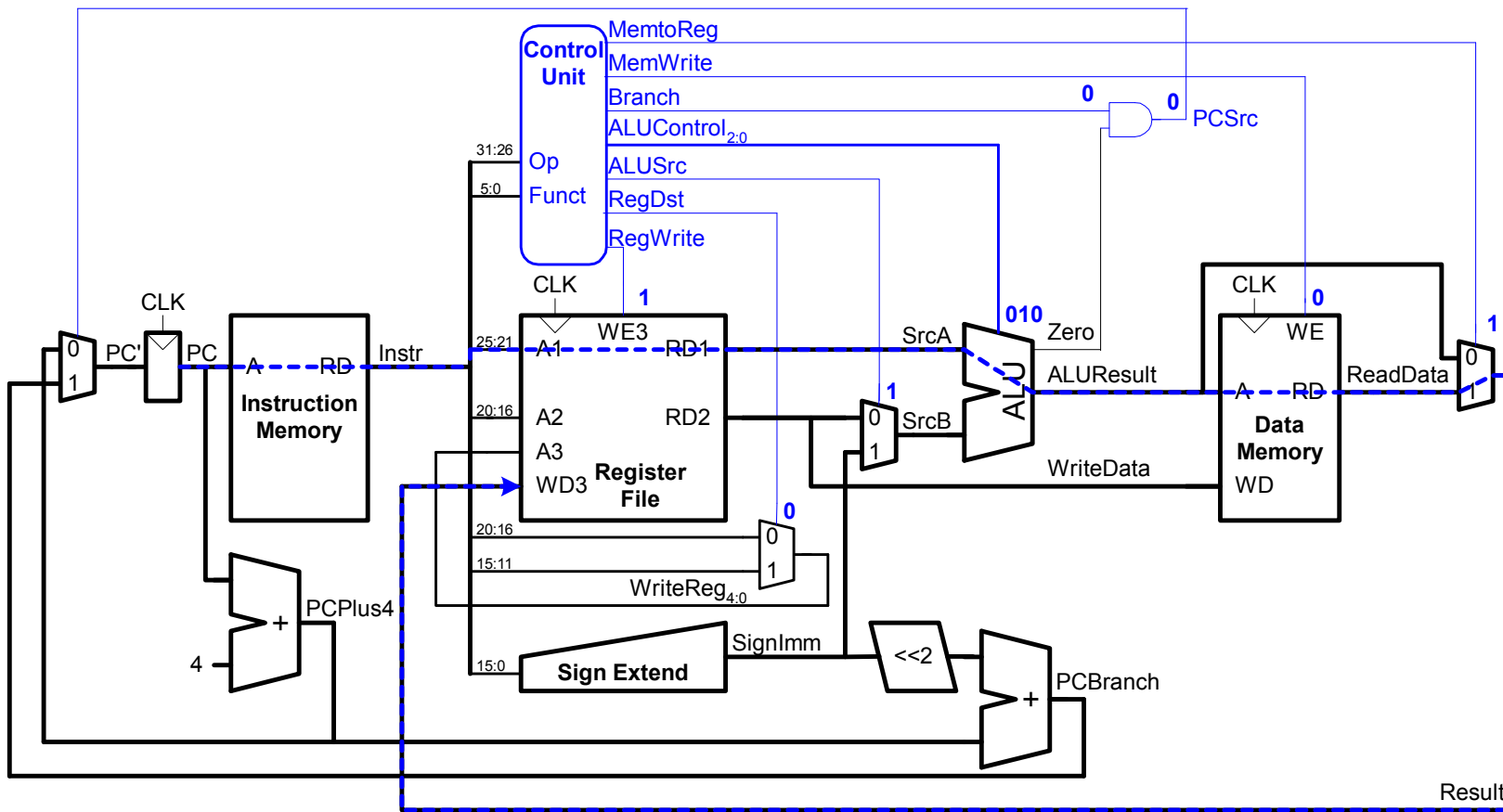

T_C limited by critical path (1w)

Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq_PC} + t_{mem} + \max(t_{RFread}, t_{sext}) + t_{mux} + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- Typically, limiting paths are:

- memory, ALU, register file

- $T_c = t_{pcq_PC} + 2t_{mem} + t_{RFread} + 2t_{mux} + t_{ALU} + t_{RFsetup}$

Single-Cycle Performance Example

| Element | Parameter | Delay (ps) |
|---------------------|---------------|------------|
| Register clock-to-Q | t_{pcq_PC} | 30 |
| Register setup | t_{setup} | 20 |
| Multiplexer | t_{mux} | 25 |
| ALU | t_{ALU} | 200 |
| Memory read | t_{mem} | 250 |
| Register file read | t_{RFread} | 150 |
| Register file setup | $t_{RFsetup}$ | 20 |

$$T_c = ?$$

Single-Cycle Performance Example

| Element | Parameter | Delay (ps) |
|---------------------|---------------|------------|
| Register clock-to-Q | t_{pcq_PC} | 30 |
| Register setup | t_{setup} | 20 |
| Multiplexer | t_{mux} | 25 |
| ALU | t_{ALU} | 200 |
| Memory read | t_{mem} | 250 |
| Register file read | t_{RFread} | 150 |
| Register file setup | $t_{RFsetup}$ | 20 |

$$\begin{aligned}T_c &= t_{pcq_PC} + 2t_{mem} + t_{RFread} + 2t_{mux} + t_{ALU} + t_{RFsetup} \\ &= [30 + 2(250) + 150 + 2(25) + 200 + 20] \text{ ps} \\ &= 950 \text{ ps}\end{aligned}$$

Single-Cycle Performance Example

Program with 100 billion instructions:


$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(950 \times 10^{-12} \text{ s}) \\ &= \mathbf{95 \text{ seconds}}\end{aligned}$$

Multicycle MIPS Processor

- **Single-cycle:**
 - + simple
 - cycle time limited by longest instruction (1_w)
 - 2 adders/ALUs & 2 memories
- **Multicycle:**
 - + higher clock speed
 - + simpler instructions run faster
 - + reuse expensive hardware on multiple cycles
 - sequencing overhead paid many times
- **Same design steps: datapath & control**


Multicycle State Elements

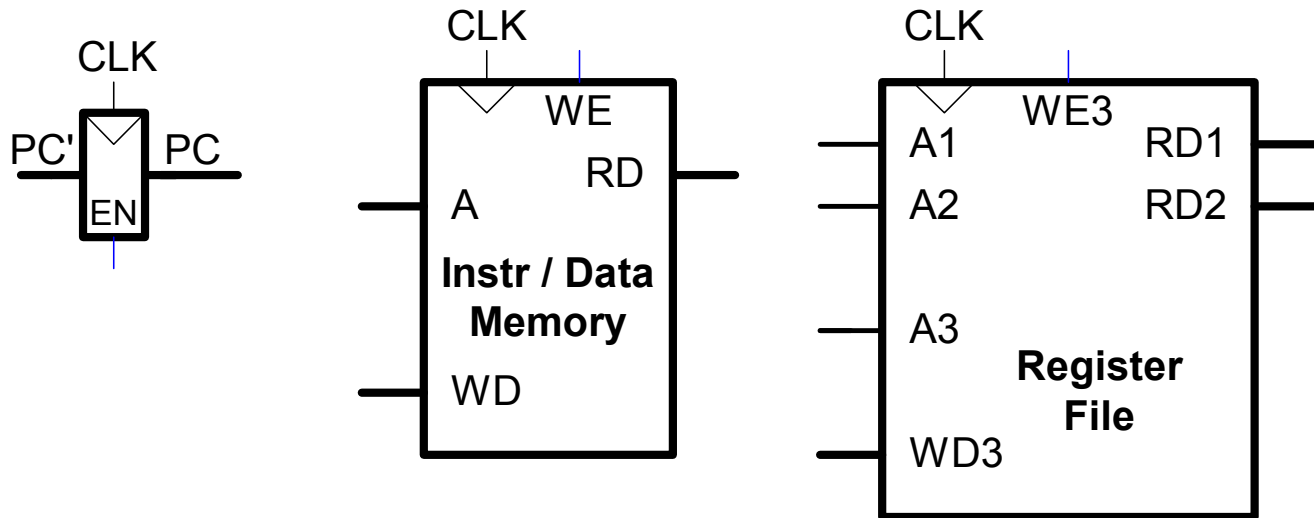- Replace Instruction and Data memories with a single unified memory – more realistic




Multicycle Datapath: Instruction Fetch

STEP 1: Fetch instruction

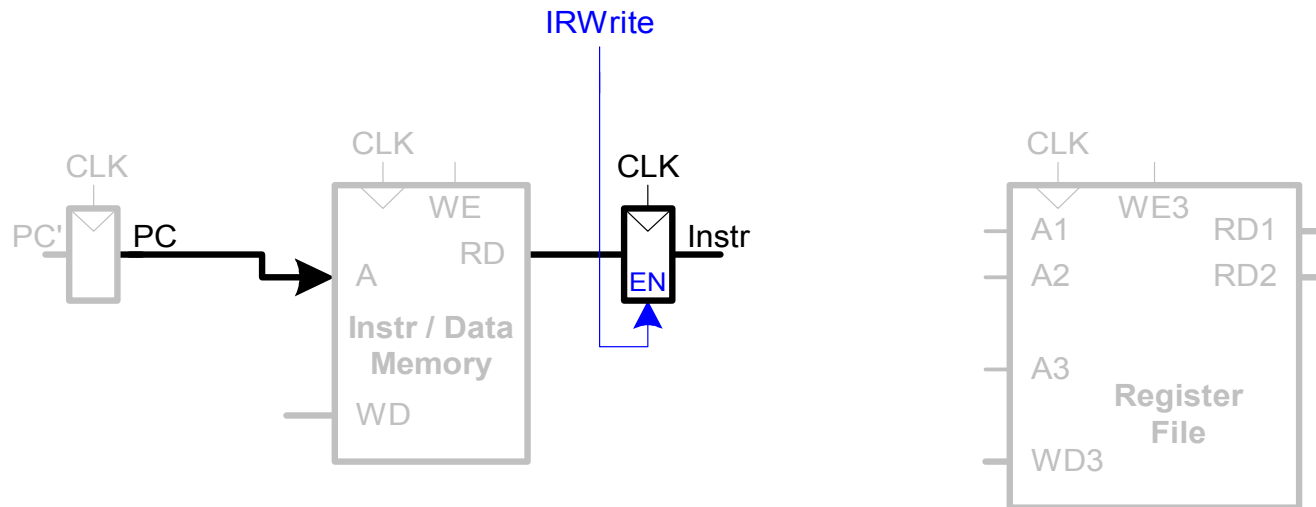


Multicycle Datapath: 1_W Register Read

STEP 2a: Read source operands from RF

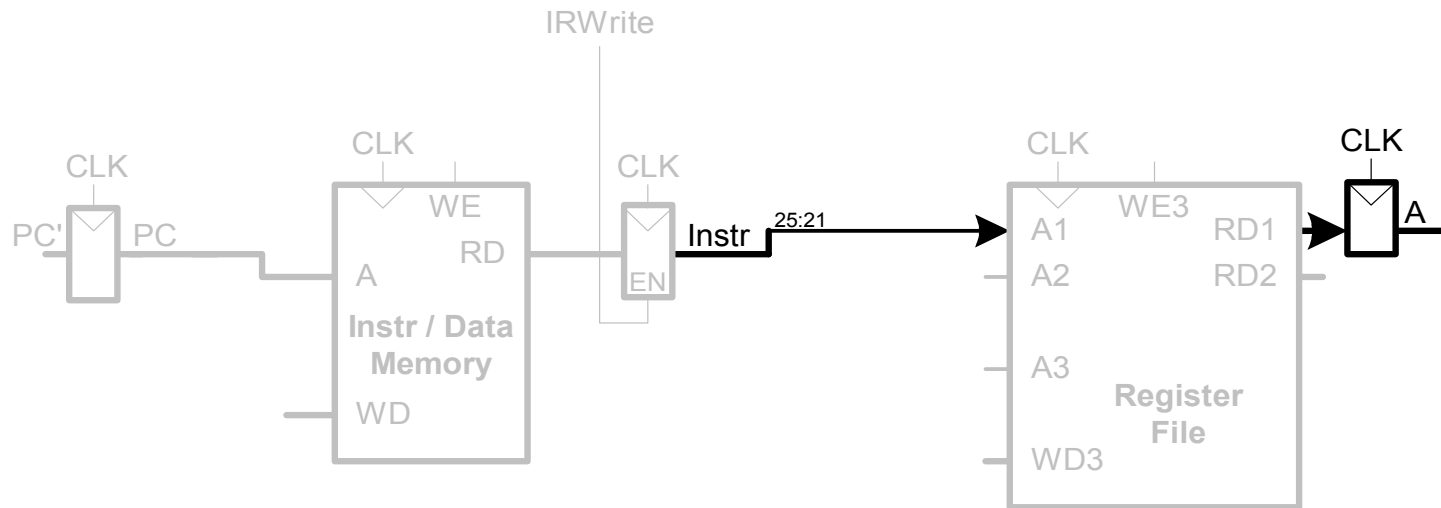


Multicycle Datapath: 1_w Immediate

STEP 2b: Sign-extend the immediate

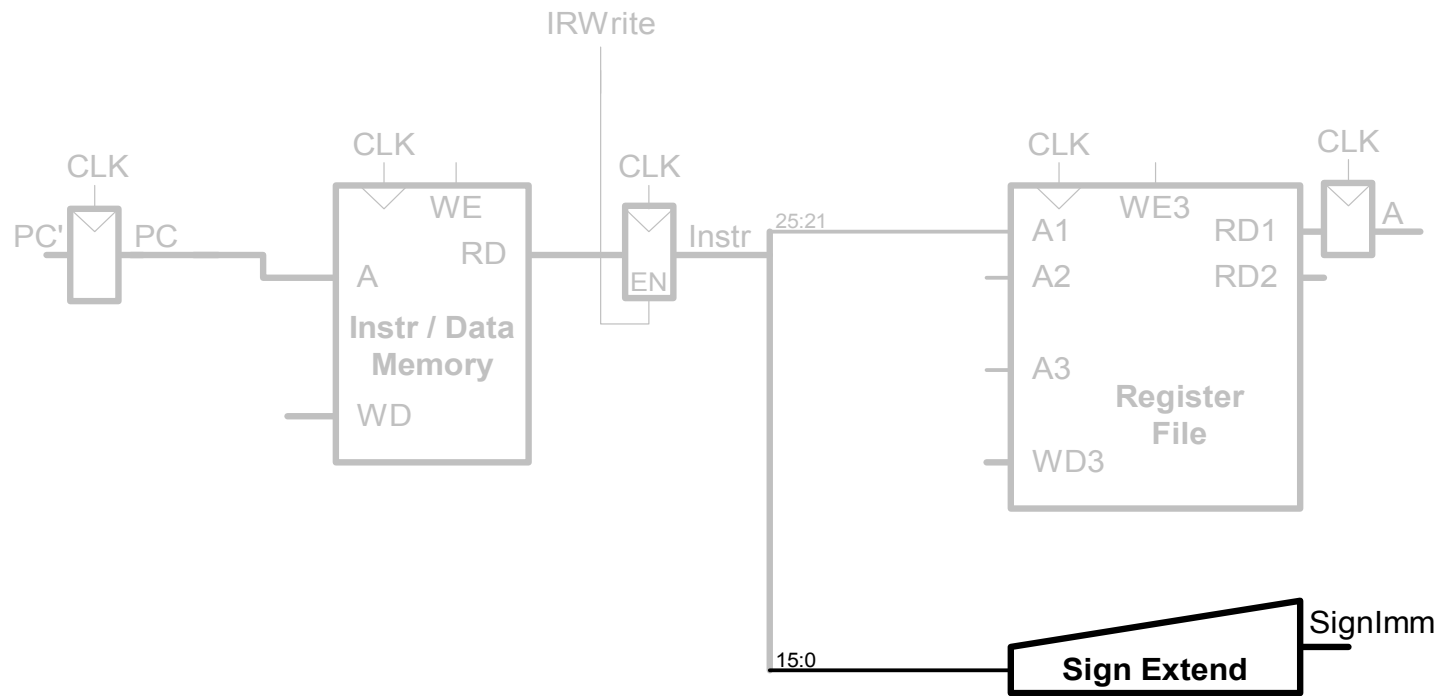


Multicycle Datapath: 1_W Address

STEP 3: Compute the memory address

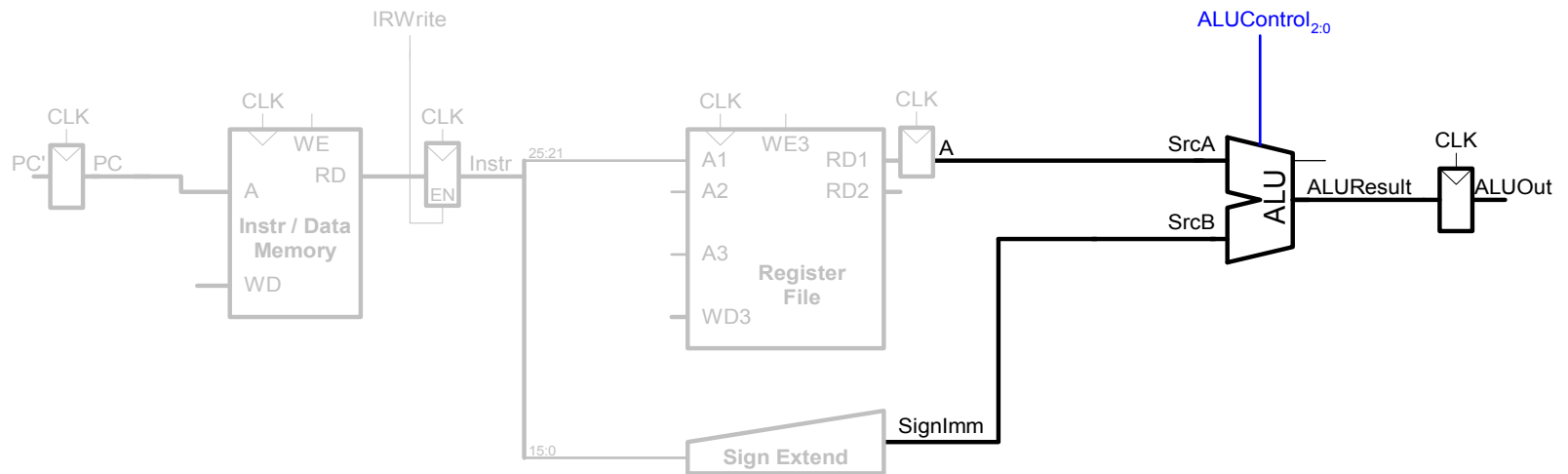


Multicycle Datapath: 1_W Memory Read

STEP 4: Read data from memory

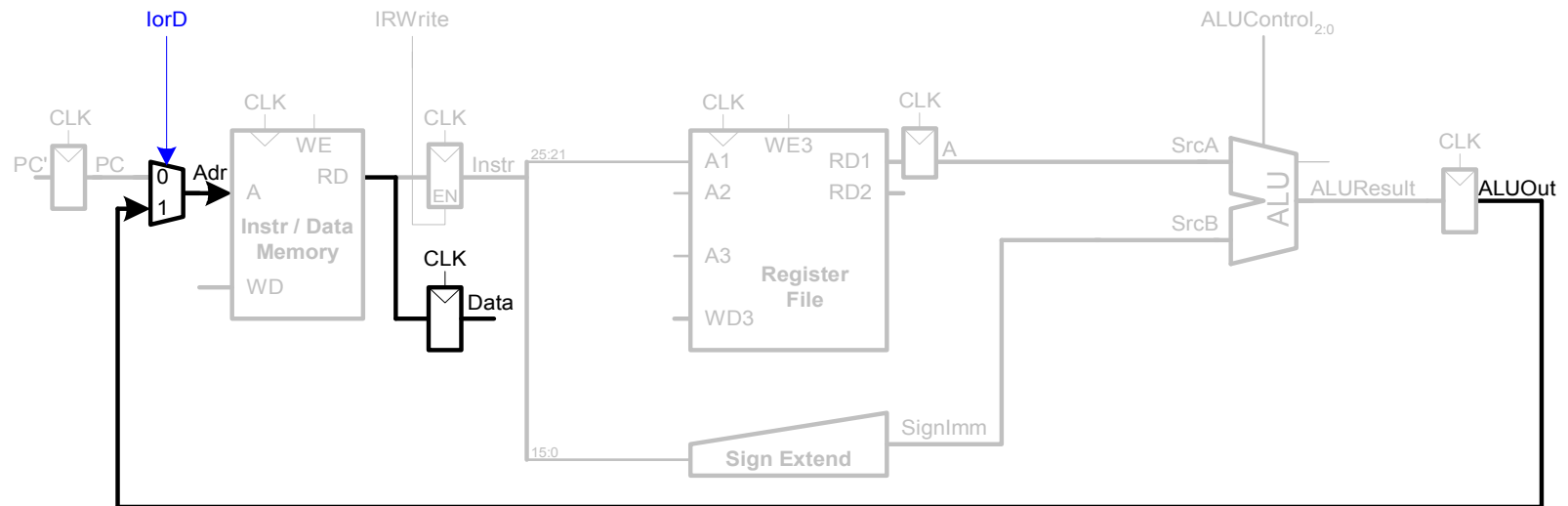


Multicycle Datapath: 1_W Write Register

STEP 5: Write data back to register file

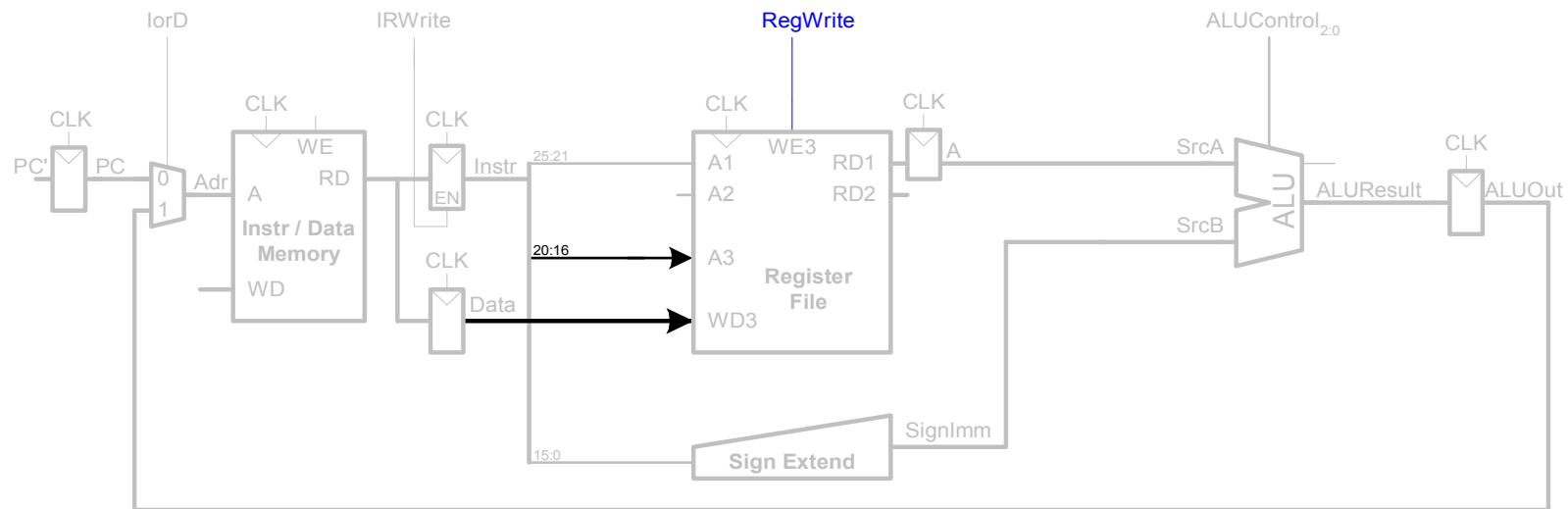


Multicycle Datapath: Increment PC

STEP 6: Increment PC

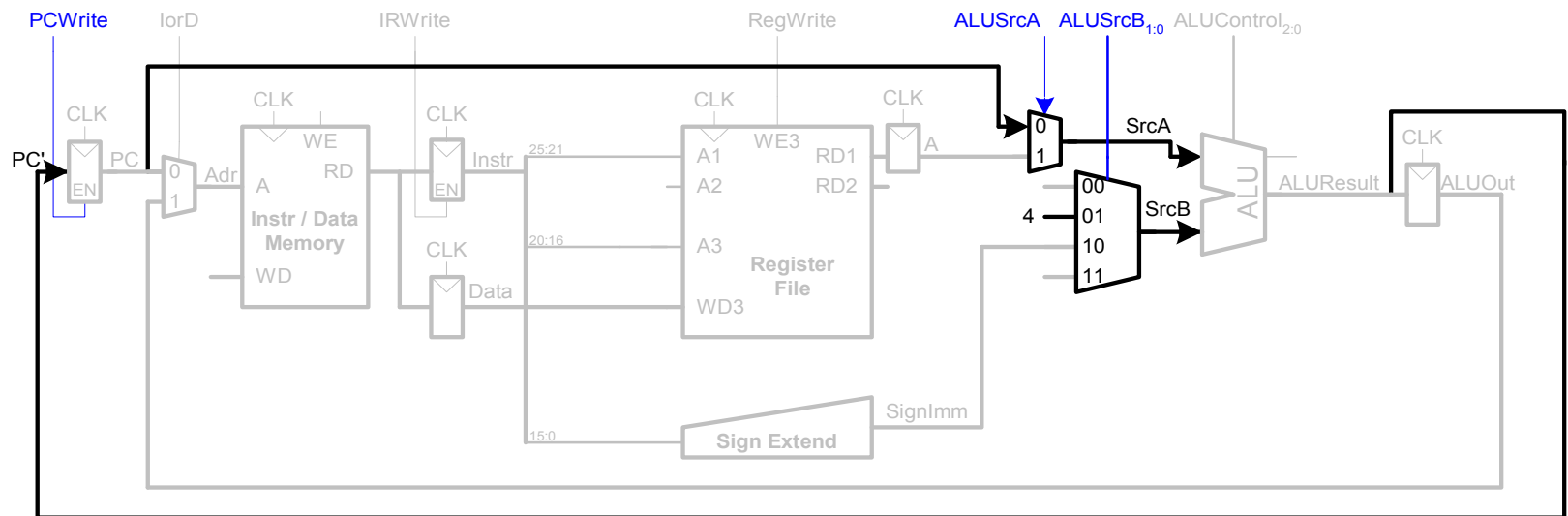


Multicycle Datapath: SW

Write data in `rt` to memory

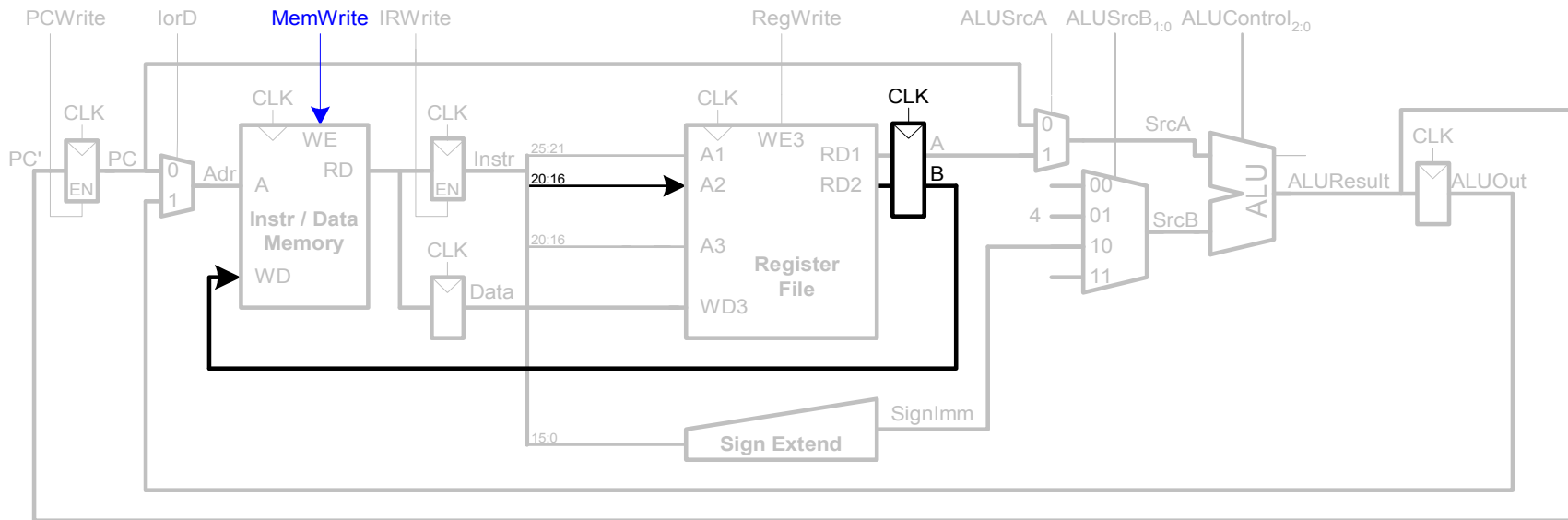


Multicycle Datapath: R-Type

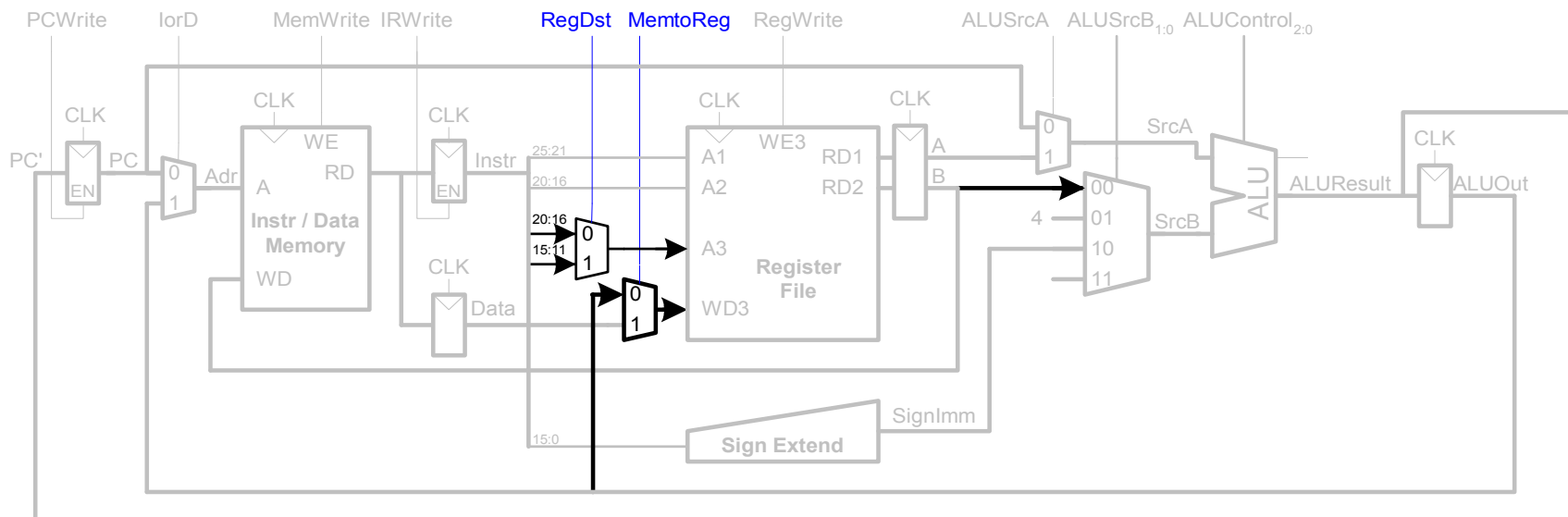- Read from rs and rt
- Write $ALUResult$ to register file
- Write to rd (instead of rt)




Multicycle Datapath: beq

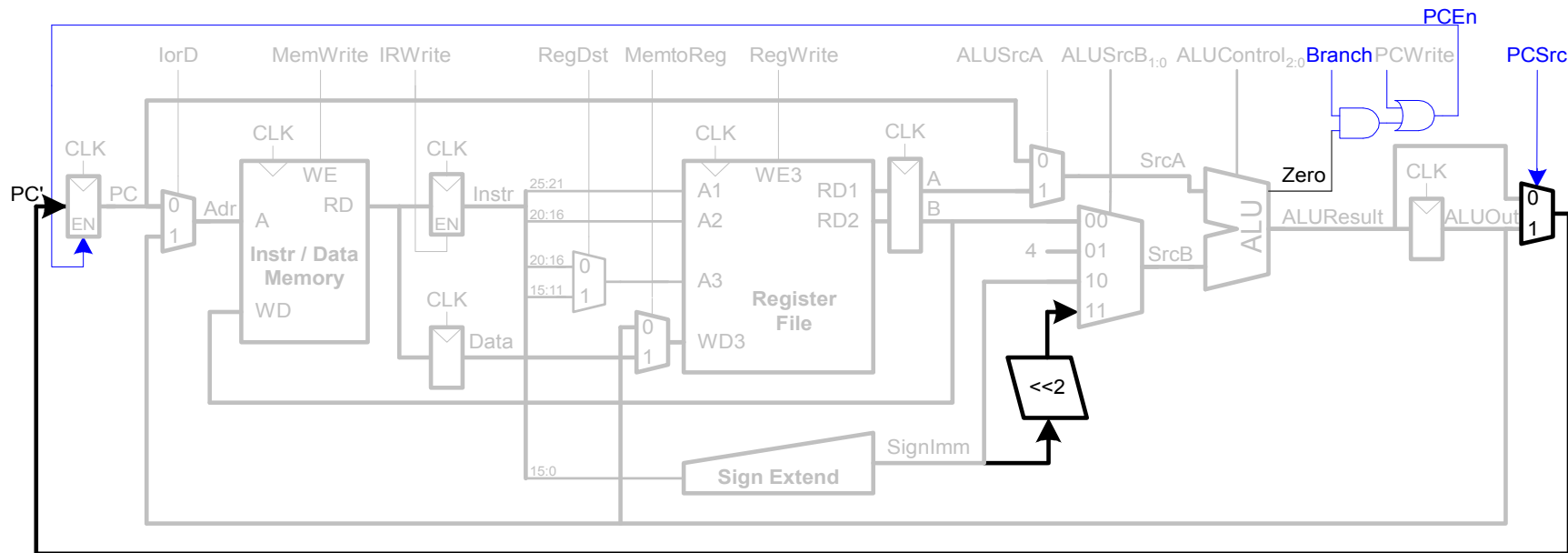
- $rs == rt?$
- $BTA = (\text{sign-extended immediate} \ll 2) + (\text{PC}+4)$



Multicycle Processor

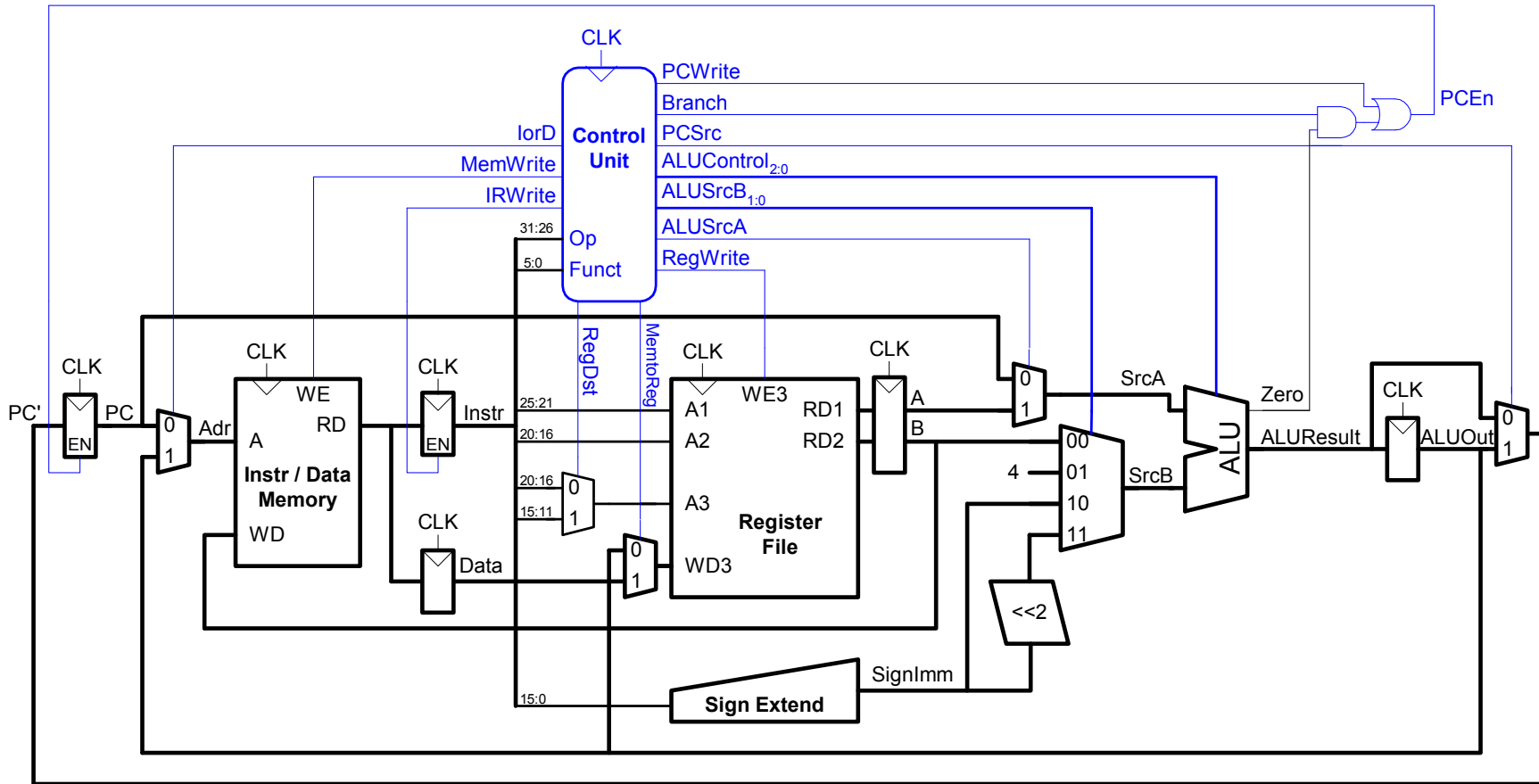

Multicycle Control

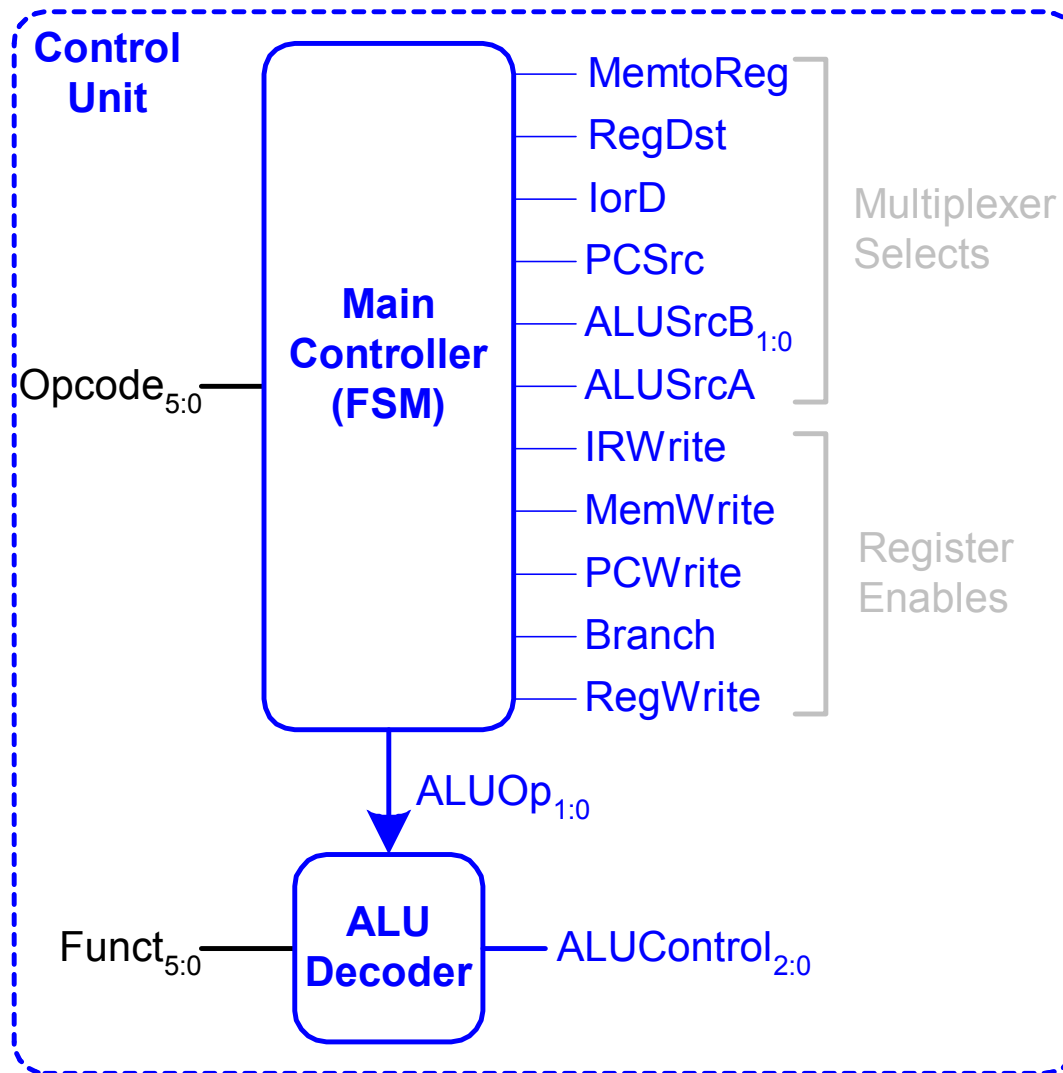

Multicycle Processor Performance


- Instructions take different number of cycles:
 - 3 cycles: beq, j
 - 4 cycles: R-Type, sw, addi
 - 5 cycles: lw
- CPI is weighted average
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 11% branches
 - 2% jumps
 - 52% R-type

$$\text{Average CPI} = (0.11 + 0.02)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$$

Multicycle Processor Performance

Multicycle critical path:
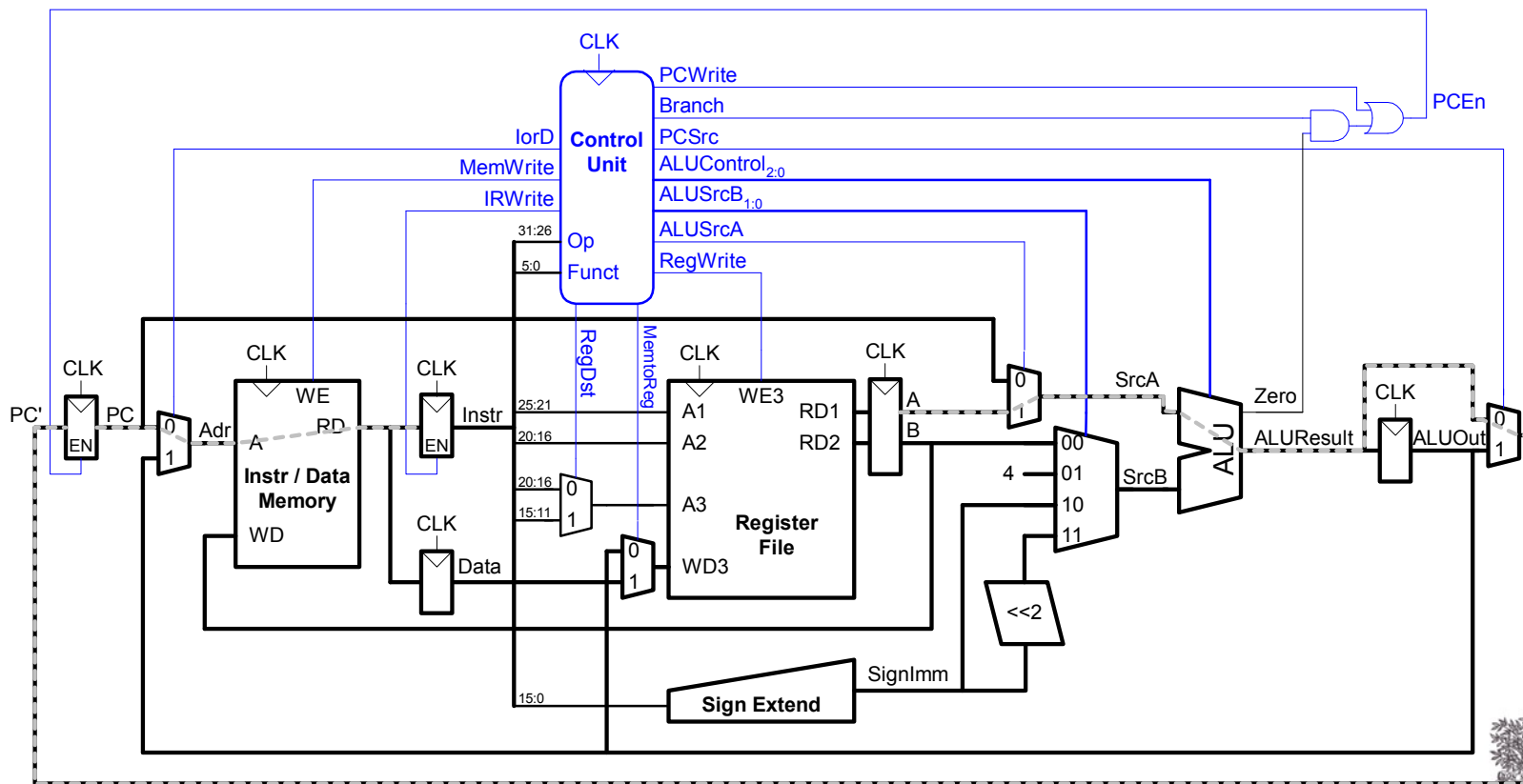
$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$



Multicycle Performance Example

| Element | Parameter | Delay (ps) |
|---------------------|---------------|------------|
| Register clock-to-Q | t_{pcq_PC} | 30 |
| Register setup | t_{setup} | 20 |
| Multiplexer | t_{mux} | 25 |
| ALU | t_{ALU} | 200 |
| Memory read | t_{mem} | 250 |
| Register file read | t_{RFread} | 150 |
| Register file setup | $t_{RFsetup}$ | 20 |

$$T_c = ?$$

Multicycle Performance Example

| Element | Parameter | Delay (ps) |
|---------------------|---------------|------------|
| Register clock-to-Q | t_{pcq_PC} | 30 |
| Register setup | t_{setup} | 20 |
| Multiplexer | t_{mux} | 25 |
| ALU | t_{ALU} | 200 |
| Memory read | t_{mem} | 250 |
| Register file read | t_{RFread} | 150 |
| Register file setup | $t_{RFsetup}$ | 20 |

$$\begin{aligned}T_c &= t_{pcq_PC} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup} \\ &= t_{pcq_PC} + t_{mux} + t_{mem} + t_{setup} \\ &= [30 + 25 + 250 + 20] \text{ ps} \\ &= \mathbf{325 \text{ ps}}\end{aligned}$$

Chapter 7 :: Topics

- For a program with 100 billion instructions executing on a multicycle MIPS processor
 - $CPI = 4.12$
 - $T_c = 325$ ps

Execution Time =

- For a program with 100 billion instructions executing on a multicycle MIPS processor
 - $CPI = 4.12$
 - $T_c = 325$ ps

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times CPI \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= 133.9 \text{ seconds}\end{aligned}$$

- This is **slower** than the single-cycle processor (92.5 seconds). Why?

Multicycle Performance Example


Program with 100 billion instructions

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= \mathbf{133.9 \text{ seconds}}\end{aligned}$$

This is **slower** than the single-cycle processor (92.5 seconds). Why?

- Not all steps same length
- Sequencing overhead for each step ($t_{pcq} + t_{\text{setup}} = 50 \text{ ps}$)

Review: Single-Cycle Processor

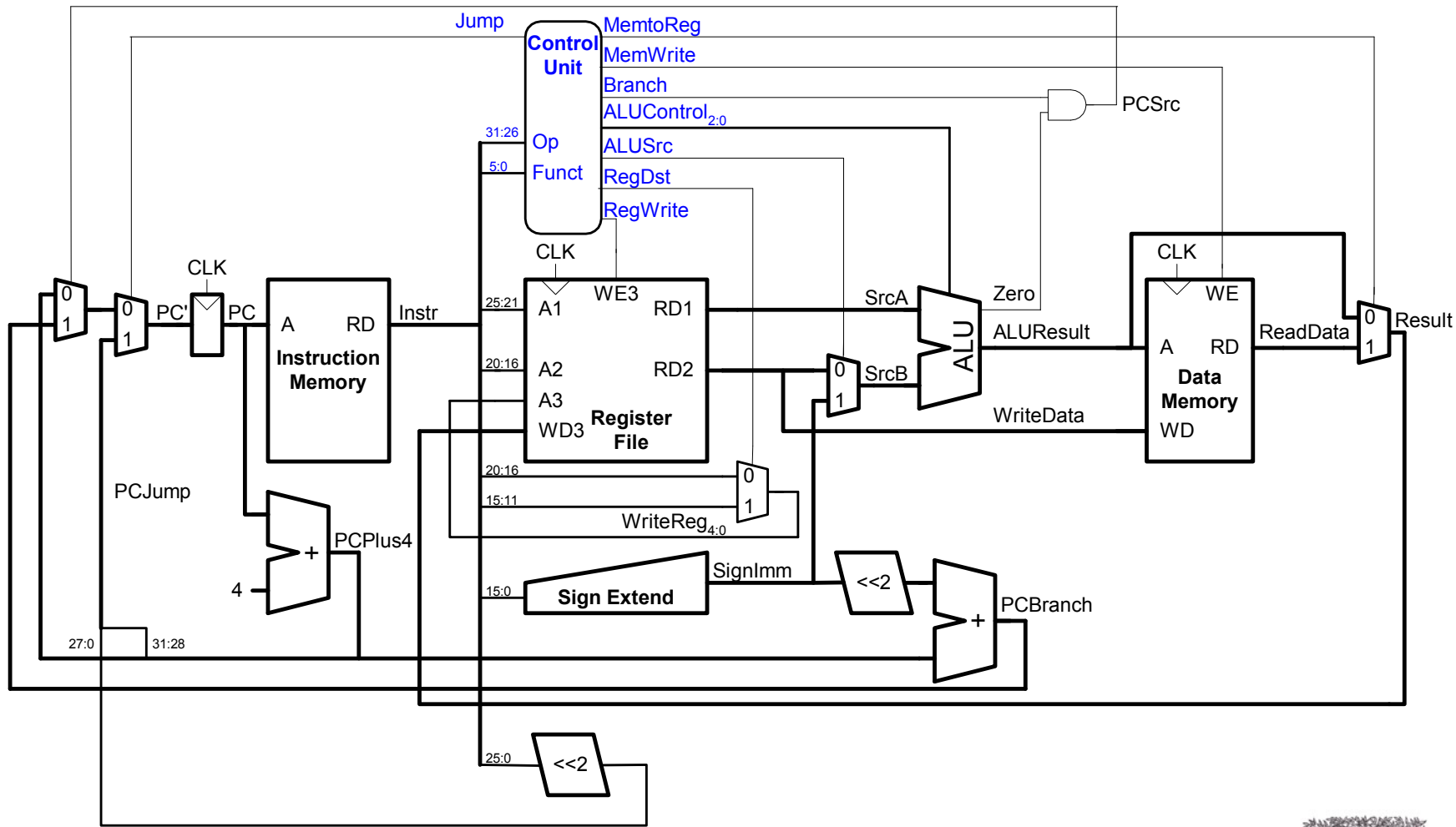

Review: Multicycle Processor

