Digital Design and Computer Architecture

David Money Harris and Sarah L. Harris



5-<1>

Copyright © 2007 Elsevier

ROM Storage

Ę١



Example: Logic with ROMs

• Implement the following logic functions using a 2² × 3-bit ROM:





5-<3>

Logic with Any Memory Array



Ð

Copyright © 2007 Elsevier

ELSEVIER

5-<6>

Multi-ported Memories

- **Port:** address/data pair
- 3-ported memory
 - 2 read ports (A1/RD1, A2/RD2)
 - 1 write port (A3/WD3, WE3 enables writing)
- Small multi-ported memories are called *register files*









- Efficiently store large amounts of data
- Three common types:
 - Dynamic random access memory (DRAM)
 - Static random access memory (SRAM)
 - Read only memory (ROM)
- An *M*-bit data value can be read or written at each unique *N*-bit address.





5-<6>

1

- Two-dimensional array of bit cells
- Each bit cell stores one bit
- An array with N address bits and M data bits:
 - 2^N rows and M columns
 - Depth: number of rows (number of words)
 - Width: number of columns (size of word)
 - Array size: depth \times width = $2^N \times M$





Memory Array: Example

- $2^2 \times 3$ -bit array
- Number of words: 4
- Word size: 3-bits
- For example, the 3-bit word stored at address 10 is 100





5-<8>





Copyright © 2007 Elsevier

5-<9>

Ð

Copyright © 2007 Elsevier



- Wordline:
 - similar to an enable
 - allows a single row in the memory array to be read or written
 - corresponds to a unique address
 - only one wordline is HIGH at any given time



Ð





5-<11>