

EC 464 – LPVLSI

Module V

Fully Complementary Logic

▶ Advantages

- Ease of design
- Low power dissipation
- Low sensitivity of noise
- Scalability


▶ Disadvantages

- Low performance for large fan in gates

➤ Requires $2N$ transistors for N input logic


- N NMOS
- N PMOS

2 input NAND

 


A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0


Depletion Load nMOS Logic

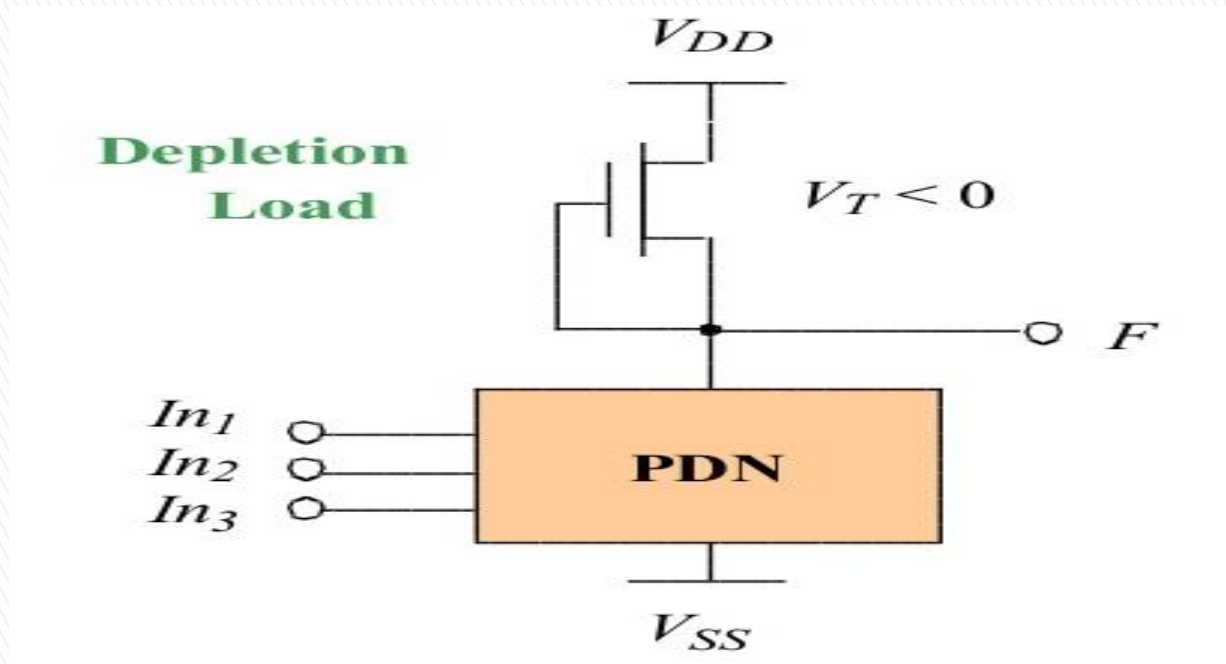


Pseudo nMOS

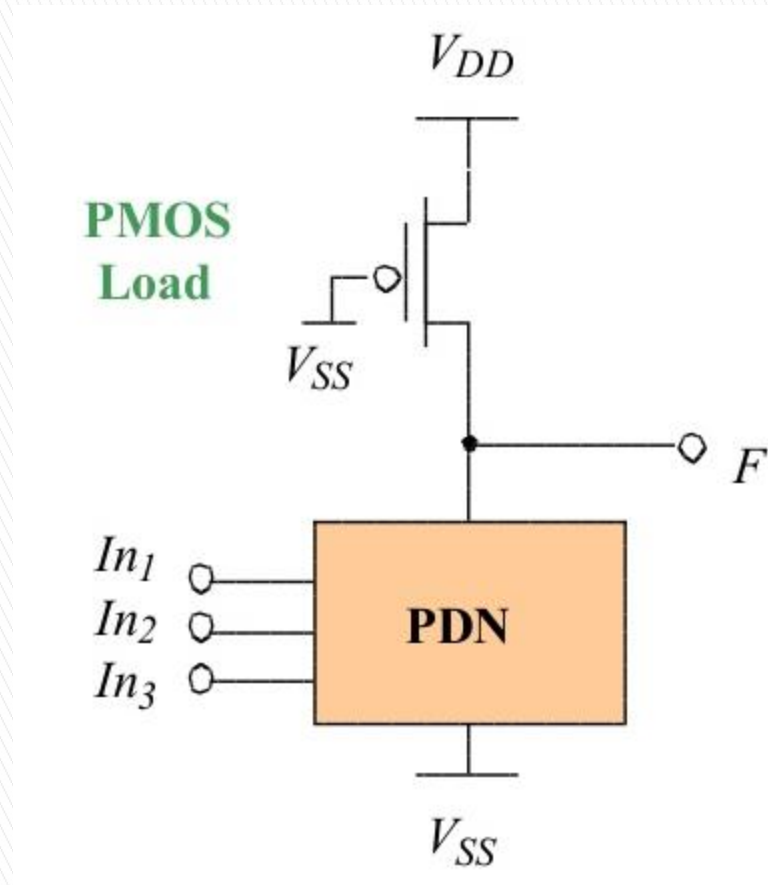

 
Differential Cascade Voltage Switch Logic (DCVS)



AND/NAND

 


Ex OR/EX NOR

 


Pass Transistor Logic

 - ▶ They are simple FETs that pass the signal between the drain and source terminals instead of a fixed power supply value
- ▶ The switch is controlled by the gate voltage V_G
- ▶ If $V_G = 0$, then the transistor is OFF and there is no connection between the input and output
- ▶ Placing a high voltage of $V_G = V_{DD}$ drives the nFET active and connects the input and output



AND implementation


 


When $B=0$, $F=0$

When $B=1$, $F=A$

A	B	F
0	0	0
1	0	0
0	1	0
1	1	1

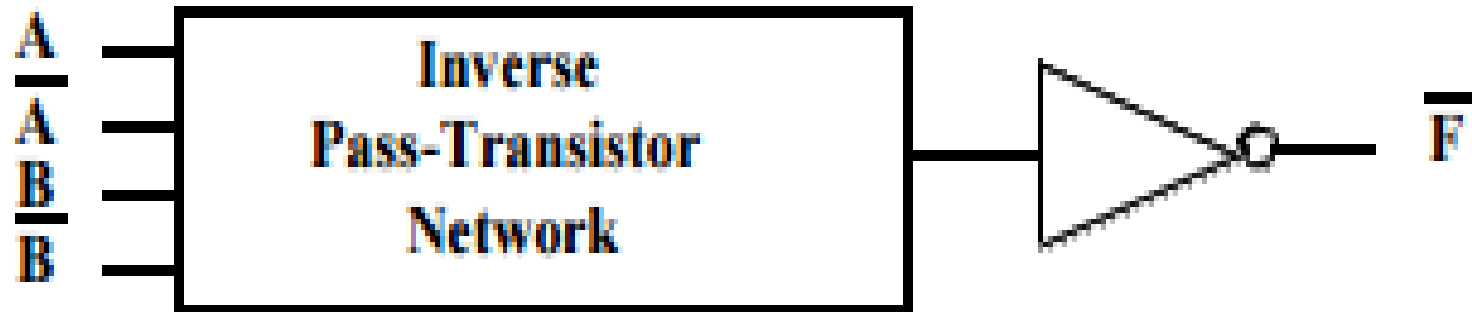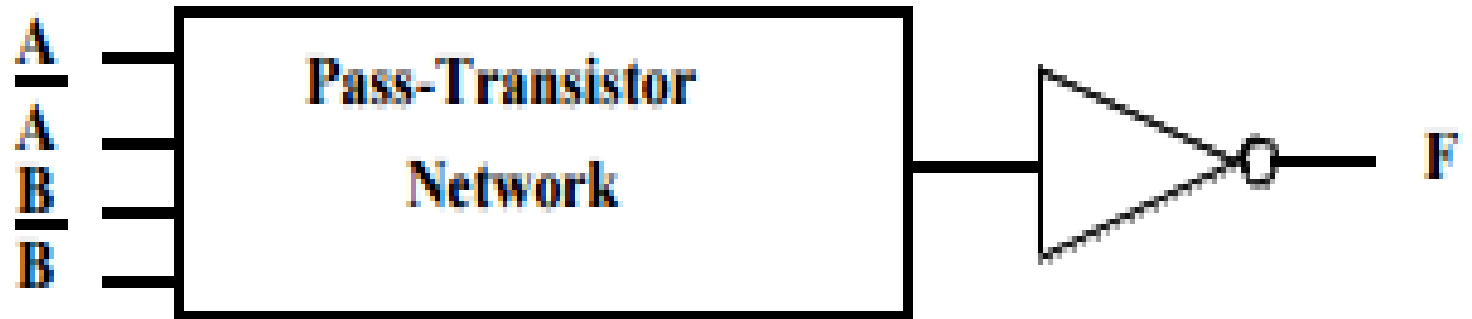
Complementary/ Differential Pass Transistor Logic (CPL/ DPL)



CPL/ DPL

- ▶ Designed for high performance
- ▶ Accept true and complementary inputs and produce true and complementary outputs
- ▶ Since the circuits are differential complementary data inputs and outputs are always available
- ▶ Since circuit is differential, complimentary inputs and outputs are available.
- ▶ Although generating differential signals require extra circuitry, complex gates such as XORs, MUXs and adders can be realized efficiently.
- ▶ CPL is a static gate, because outputs are connected to V_{DD} or GND through a low-resistance path (high noise resilience).
- ▶ Design is modular – all gates use same topology; only inputs are permuted. This facilitates the design of a library of gates

AND/NAND

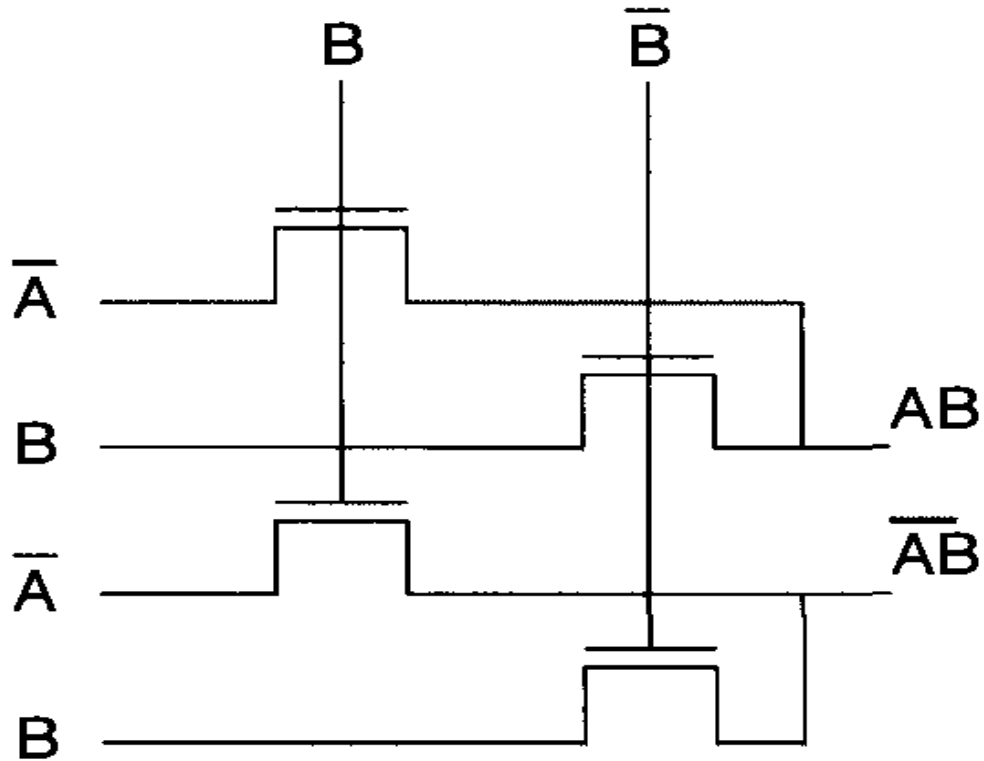

- ▶ Differential pass-transistor logic suffers from the problem of
 - ✓ Static power dissipation
 - ✓ Reduced noise margin.
- ▶ There are several solutions are proposed to deal with such problems-

1. Level Restoration
2. Multiple-Threshold Transistor
3. Transmission gate logic