 


EC 464 – LPVLSI

Module IV

Dynamic Gate


$$\text{Out} = \overline{\text{CLK}} + ((\overline{AB}) + C) \cdot \text{CLK}$$



Two phase operation

Precharge ($\text{Clk} = 0$)

Evaluate ($\text{Clk} = 1$)

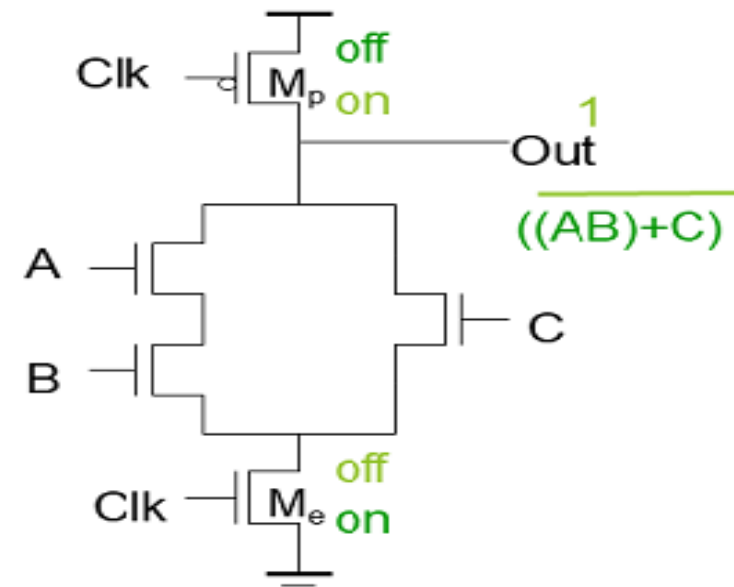

- The logic is implemented using N type gates

Precharge phase

- ▶ When $CLK = 0$, the output node OUT is precharged to V_{DD} by the PMOS transistor M_p
- ▶ During that time, nMOS M_e is OFF and the pull down path is disabled
- ▶ The input voltages are applied during this phase but they have no influence on the output level since M_e is turned OFF
- ▶ The evaluation FET eliminates any static power that would be consumed during the precharge period

Evaluation

- ▶ When $CLK=1$, the precharge transistor M_p is turned OFF and the evaluation transistor M_e is turned ON
- ▶ The output is conditionally discharged based on the input values and the pull down topology
- ▶ If the inputs are such that the PDN conducts, a low resistance path exists between OUT and GND and the output is discharged to ground
- ▶ If the PDN is turned OFF, the output value remains at V_{DD} and remains stored on the output capacitance

Domino NAND

